

## 九十九學年四技二專第二次聯合模擬考試 電機與電子群 專業科目 (一) 詳解

99-2-03-4  
99-2-04-4

1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16	17	18	19	20	21	22	23	24	25
A	D	A	C	D	C	C	A	A	C	B	D	A	D	B	A	C	A	D	B	D	A	B	C	C
26	27	28	29	30	31	32	33	34	35	36	37	38	39	40	41	42	43	44	45	46	47	48	49	50
D	B	C	D	C	A	B	A	D	A	D	C	B	C	B	A	B	A	D	B	C	D	B	D	A

### 第一部份：基本電學

1.  $\frac{P_o}{500} = \eta_2 = 0.85 \Rightarrow P_o = 425 \text{ W}$

$\frac{P_o}{P_i} = \eta_1 \times \eta_2 \Rightarrow \frac{425}{P_i} = 0.7 \times 0.85 \Rightarrow P_i \doteq 714 \text{ W}$


$\therefore P_{\text{loss}} = 714 - 425 \doteq 290 \text{ W}$

2. 長度拉長 3 倍  $\Rightarrow$  截面積縮小為  $\frac{1}{3}$  倍

$R' = \rho \cdot \frac{3 \cdot \ell}{\frac{1}{3}A} = 9 \cdot \rho \cdot \frac{\ell}{A} = 9R$

3.  $\begin{cases} R_2 = R_o \cdot [1 + \alpha_o \cdot t_2] \\ R_1 = R_o \cdot [1 + \alpha_o \cdot t_1] \end{cases} \Rightarrow \frac{1.5}{1} = \frac{1 + \alpha_o \cdot 70}{1 + \alpha_o \cdot 20} \Rightarrow \alpha_o = \frac{1}{80}$

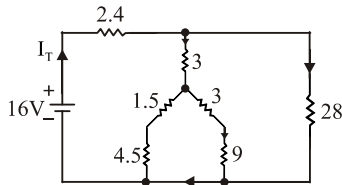4.  $I_T = \frac{16}{2.4 + (7 // 28)} = 2 \text{ A}$




5.  $I_T = \frac{36}{2 + [(3 // 6) + 6] // 8} = 6 \text{ A}$


$I_1 = 6 \text{ A} \times \frac{8}{8 + 8} = 3 \text{ A}$

$I_2 = 3 \text{ A} \times \frac{6}{3 + 6} = 2 \text{ A}$

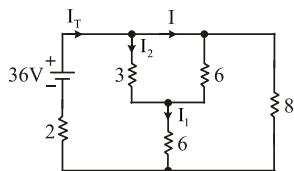$\therefore I = I_T - I_2 = 6 - 2 = 4 \text{ A}$



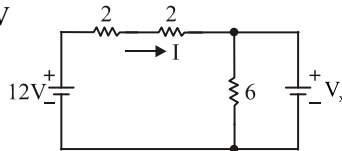
6.  $V_x = 12 - 2 \times (2 + 2) = 4 \text{ V}$



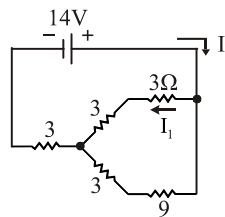7.  $I = \frac{14}{3 + (6 // 12)} = 2 \text{ A}$

$I_1 = 2 \text{ A} \times \frac{12}{6 + 12} = \frac{4}{3} \text{ A}$

$\therefore P_{3\Omega} = \left(\frac{4}{3}\right)^2 \times 3\Omega = \frac{16}{3} \text{ W}$




8.  $R_{th} = 6 // 2 = \frac{3}{2} \Omega$

$V_{th} = 3 \text{ V}$

當  $R_L = R_{th} = \frac{3}{2} \Omega$



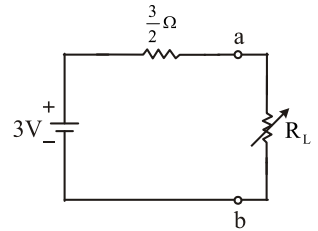
則  $P_{\text{max}} = \frac{3^2}{4 \times \frac{3}{2}} = 1.5 \text{ W}$



9.  $I_1 = \sqrt{\frac{20}{5}} = 2 \text{ A}$ ,  $I_2 = \sqrt{\frac{10}{10}} = 1 \text{ A}$

故  $I_1 > I_2 \Rightarrow 5 \Omega / 20 \text{ W}$  耐電流較大

10.

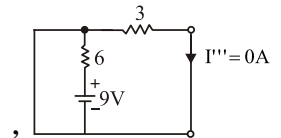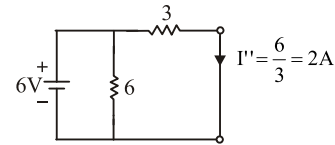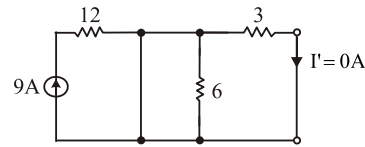

$\therefore I_N = I' + I'' + I''' = 2 \text{ A}$

11.  $Q_T = 150 \times [(6 + 3) // 18 + 9] // 30 = 1500 \mu\text{C}$

$Q_{18\mu\text{F}} = 1500 \mu\text{C} \times \frac{[(6 + 3) // 18]}{9 + [(6 + 3) // 18]} = 600 \mu\text{C}$

$Q_{3\mu\text{F}} = 600 \mu\text{C} \times \frac{3}{6 + 3} = 200 \mu\text{C}$


12.  $E_A = \frac{F}{Q} = \frac{5 \times 10^{-2}}{2 \times 10^{-5}} = 2.5 \times 10^3 \text{ V/m}$

13.  $L_T = L_1 + L_2 + L_3 + 2 \text{ M} - 2 \text{ M} - 2 \text{ M}$   
 $= 6 + 3 + 2 - 2 \times 2 = 7 \text{ H}$

$W_{L_T} = \frac{1}{2} L_T \times I^2 = \frac{1}{2} \times 7 \times 5^2 = 87.5 \text{ J}$

14.  $e_{ab} = -5 \times \frac{4 - 2}{1} = -10 \text{ V}$ ,  $e_{cd} = -3 \times \frac{4 - 2}{1} = -6 \text{ V}$

16. SW  $\rightarrow$  1

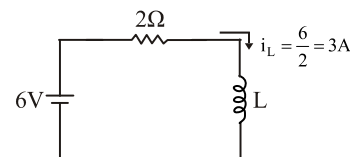


SW → 2


$$i_L(t) = 3 \cdot e^{-2t} \quad (\tau = \frac{1}{2} \text{ sec})$$

$$\therefore V_o = -2 \times i_L(t) = -6 \cdot e^{-2t}$$

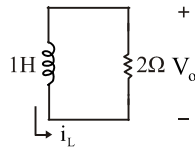
$$\therefore t = 1 \text{ sec} \Rightarrow V_o = -6 \times e^{-2} = -0.81 \text{ V}$$



17. SW 打開前：

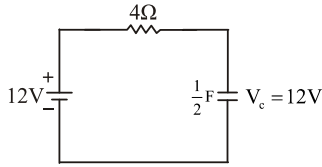

SW 打開後：

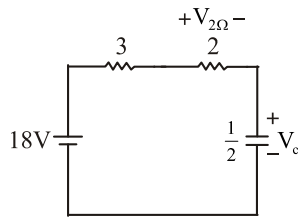


$$\tau = (3 + 2) \times \frac{1}{2} = 2.5 \text{ sec}$$

$$V_c = 12 \cdot e^{-\frac{1}{2.5}t} + 18(1 - e^{-\frac{1}{2.5}t}) \text{ (V)}$$

$$V_{2\Omega} = (18 - V_c) \times \frac{2}{3 + 2} = \frac{12}{5} \cdot e^{-\frac{1}{2.5}t}$$


$$\therefore t = 5 \text{ sec} \quad \therefore V_{2\Omega} = 2.4 \cdot e^{-2} \text{ (V)}$$

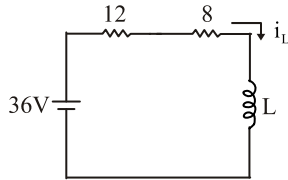18. ① SW 閉合前  $\Rightarrow i_L = 1.8 \text{ A}$



② SW 閉合(瞬間)

$$V_L = 8 \times i_L = 14.4 \text{ V}$$

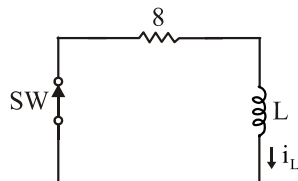

19.  $i(t) = 5 \sin 314 t \text{ (A)}$

$$V(t) = -40 \cos(314t + 30^\circ) = 40 \cdot \sin(314t - 60^\circ) \text{ (V)}$$

(A)  $f = 50 \text{ Hz}$

(B) 電路呈電容性

$$(C) \bar{Z} = \frac{\bar{V}}{\bar{I}} = \frac{40 \angle -60^\circ}{\frac{5}{\sqrt{2}} \angle 0^\circ} = 8 \angle -60^\circ \Omega$$

$$20. V_{\text{rms}} = \sqrt{\frac{(\frac{2}{\sqrt{3}})^2 \times 2 + 3^2 \times 1 + (-1)^2 \times 1 + (\frac{1}{\sqrt{3}})^2 \times 2}{6}}$$

$$= \frac{2\sqrt{5}}{3} \text{ V}$$

21.  $i_{1(t)} = 10 \cdot \sin 50 t$  ,  $i_{2(t)} = 10 \cdot \sin(50 t + 90^\circ)$

$$I_1 + I_2 = \frac{10}{\sqrt{2}} \angle 0^\circ + j \frac{10}{\sqrt{2}} = 10 \angle 45^\circ \text{ A}$$

$$(I_1 + I_2)_{\text{max}} = 10\sqrt{2} \text{ A}$$

$$22. \text{PF} = 0.6 = \frac{Z}{R} = \frac{j \cdot R \cdot X_L}{R + j \cdot X_L} \Rightarrow 0.6 = \frac{jX_L}{16 + jX_L}$$

$$\Rightarrow 9.6 + j \cdot 0.6 \cdot X_L = jX_L \Rightarrow \sqrt{9.6^2 + (0.6X_L)^2} = X_L$$

$$\Rightarrow 9.6^2 + 0.36X_L^2 = X_L^2 \Rightarrow X_L = 12 \Omega$$

$$23. \bar{I} = \frac{\bar{V}_C}{-jX_C} = \frac{30 \angle -30^\circ}{-j3} = 10 \angle 60^\circ \text{ A}$$

$$\bar{V} = \bar{I} \times \bar{Z} = 10 \angle 60^\circ \times (4 - j3) = 10 \angle 60^\circ \times 5 \angle -37^\circ = 50 \angle 23^\circ \text{ (V)}$$

$$\therefore V(t) = 50\sqrt{2} \cdot \sin(377t + 23^\circ) \text{ (V)}$$

$$= 50\sqrt{2} \cos(377t - 67^\circ) \text{ (V)}$$

$$24. \bar{Z} = 0.5 + j3.5 + [(4 - j3) // (3 + j4)]$$

$$= 0.5 + j3.5 + 3.5 + j0.5 = 4 + j4 = 4\sqrt{2} \angle 45^\circ \Omega$$

$$\therefore \bar{I}_T = \frac{\bar{V}}{\bar{Z}} = \frac{100}{4\sqrt{2} \angle 45^\circ} = \frac{25}{\sqrt{2}} \angle -45^\circ \text{ A}$$

25. ① SW 閉合前

$$0.6 = \frac{R}{Z} = \frac{12}{Z} \Rightarrow Z = 20 \Omega$$

$$\therefore |12 - jX_C| = 20 \Rightarrow X_C = 16 \Omega$$

② SW 閉合後

$$Z = 20 \Omega = 12 \pm jX \Rightarrow X = 16 \Omega$$

$$\therefore (jX_L // -j16) = \pm jX = \pm j16 \Rightarrow \frac{16 \cdot X_L}{(X_L - 16)} = \mp 16$$

$$\Rightarrow X_L = \mp(X_L - 16) = \pm(16 - X_L) \text{ (取+)}$$


$$2X_L = 16 \Rightarrow X_L = 8 \Omega$$

### 第二部份：電子學

$$26. \begin{cases} 20\% = \frac{T_p}{T} \times 100\% \\ T_p = 1 \mu\text{s} \end{cases}$$

$$\Rightarrow \frac{1 \mu\text{s}}{T} = 0.2 \Rightarrow T = 5 \mu\text{s}$$
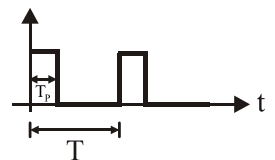
$$\therefore f = \frac{1}{T} = 200 \text{ kHz}$$




27. (B) 二極體在逆向偏壓時為過渡電容，範圍約為數 PF；順向偏壓時為擴散電容，範圍約為數  $\mu\text{F}$


28. 原電路等效

$$I_D = \frac{1 - 0.6}{100} = 4 \text{ mA}$$

$$P_D = I_D \times V_D$$

$$= 4 \times 0.6 = 2.4 \text{ mW}$$

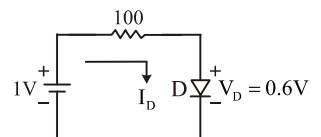

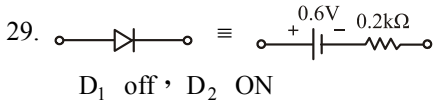

$$\therefore V_o = \frac{\frac{2}{1.5} + \frac{5}{8.5}}{\frac{1}{1.5} + \frac{1}{8.5}} = 2.45 \text{ V}$$

30. 二次側峰值  $V_{2m} = \frac{110\sqrt{2}}{5} = 22\sqrt{2} \text{ V}$

(半波)  $V_{(av)} = (\frac{V_{2m}}{\pi} - 0.6) \times \frac{2}{1+2}$   
 $= (\frac{22\sqrt{2}}{\pi} - 0.6) \times \frac{2}{3} = 6.2 \text{ V}$

31.  $V_{2m} = \frac{110\sqrt{2}}{10} = 11\sqrt{2} \text{ V}$ ,  $V'_{2m} = \frac{1}{2} V_{2m} = \frac{11\sqrt{2}}{2} \text{ V}$

$$V_A = \frac{2}{\pi} V'_{2m} \times \frac{5}{5+10} = \frac{11\sqrt{2}}{\pi} \times \frac{1}{3} = 1.65 \text{ V}$$

32. ①  $V_i > 0$  (正半週)

$$V_o = 10 \times \frac{3.3}{2.2+3.3} = 6 \text{ V} \Rightarrow D \text{ ON}, \therefore V_{o(max)} = +5.5 \text{ V}$$

②  $V_i < 0$  (負半週)  $\Rightarrow D$  off

$$V_{o(min)} = -10 \times \frac{3.3}{2.2+3.3} = -6 \text{ V}$$

③  $\Delta V_o = V_{o(max)} - V_{o(min)} = 5.5 - (-6) = 11.5 \text{ V}$

33.  $V_o = -4 \sim +16 \text{ V}$

34.  $I_C = \beta I_B + (1+\beta)I_{CBO}$ ,  $\beta = \frac{\alpha}{1-\alpha} = \frac{0.99}{1-0.99} = 99$

$$\therefore I_C = 99 \times 15 + (1+99) \times 5 \mu\text{A} = 1985 \mu\text{A} = 1.985 \text{ mA}$$

37.  $I_B = \frac{2-0.7-(-2)}{2+(1+100) \times 0.5} \doteq 0.063 \text{ mA}$

$$I_C = 100 \times I_B = 6.3 \text{ mA}$$


$$V_{CE} = -18 + (2+0.5) \times 6.3 - 2 \doteq -4.3 \text{ V}$$

38.  $V_C = 12 - 2 \times (I_B + \frac{0.7}{20} + 99I_B)$

$$= 100 \times (I_B + \frac{0.7}{20}) + 0.7$$

$$\Rightarrow I_B = 0.0257 \text{ mA}$$

$$\therefore V_C \doteq 6.8 \text{ V}$$

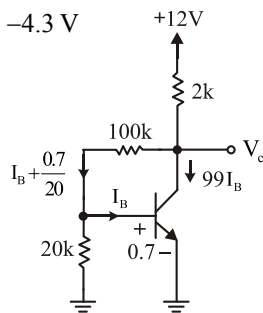

39.  $V_C = 16 - 2 \times (2 + \frac{2}{100})$

$$= 250 \times (\frac{2}{100}) + 0.7 + (2 + \frac{2}{100}) \times R_E$$

$$\Rightarrow 11.96 = 5.7 + 2.02R_E \Rightarrow R_E \doteq 3.1 \text{ k}\Omega$$

40. (1) 有  $C_E$ :  $Z_i = 90 // 10 // 3 = 2.25 \text{ k}\Omega$

(2) 無  $C_E$ :  $Z_i = 90 // 10 // (3 + 101 \times 1) \doteq 8.3 \text{ k}\Omega$

41. (A) 共基極(CB)具有極低輸入阻抗與極高輸出阻抗

42.  $I_E = \frac{10.7-0.7}{5} = 2 \text{ mA}$ ,  $r_e = \frac{V_T}{I_E} = \frac{25 \text{ mV}}{2 \text{ mA}} = 12.5 \Omega$

$$A_V = +\alpha \cdot \frac{R_C}{r_e} \doteq \frac{2 \text{ k}}{12.5} = 160$$

$$\therefore V_{o(P-P)} = A_V \times V_{i(P-P)} = 0.32 \text{ V}$$

43.  $-40 = 10 \cdot \log(\frac{P_o}{1 \text{ mW}})$

$$\therefore \frac{P_o}{1 \text{ mW}} = 10^{-4} \Rightarrow P_o = 10^{-7} \text{ W} = 0.1 \mu\text{W}$$

44.  $A_i = \frac{I_o}{I_i} = 800 = (1+\beta_1) \times (1+\beta_2) \times \frac{3}{3+6}$

$$\therefore \beta_1 = 39, \beta_2 = 59$$

45.  $A_{VS} = \frac{V_o}{V_s} = \frac{V_o}{V_b} \times \frac{V_b}{V_s} = -\beta \times \frac{3//6}{2} \times \frac{(40//10//2)}{0.4+(40//10//2)}$

$$= -250 \times \frac{1.6}{2} = -200$$

46.  $\begin{cases} \text{NEMOS: } V_{GS} > V_t, V_{GD} \leq V_t (\text{夾止區}) \\ \text{PDMOS: } V_{GS} < V_p, V_{GD} \geq V_p (\text{夾止區}) \end{cases}$

$$\Rightarrow \begin{cases} 3 \text{ V} < V_G \leq 6.5 \text{ V} (\text{NEMOS}) \\ 3 \text{ V} \leq V_G < 5.5 \text{ V} (\text{PDMOS}) \end{cases}$$

$$\therefore V_G = 4.5 \text{ V} \text{ 符合}$$

47. (A) CS  $\rightarrow$  反相

(B) CD  $\rightarrow$  極高輸入阻抗, 極低輸出阻抗

(C) CD  $\rightarrow$  源極隨耦器

48. (B) CMOS: 交換速度慢

49.  $I_D = 8 = k(2.5-0.5)^2 \Rightarrow k = 2 \text{ mA/V}^2$

$$I_D = 2 \times (3.5-0.5)^2 = 18 \text{ mA}$$

50.  $I_{DQ} = I_{DSS}(1 - \frac{V_{GS}}{V_p})^2 \Rightarrow 3 = 12 \times (1 - \frac{V_{GS}}{-4})^2$

$$\therefore V_{GS} = -2 \text{ V}$$

$$g_m = \frac{2 I_{DSS}}{-V_p} \times (1 - \frac{V_{GS}}{V_p}) = \frac{2 \times 12}{4} \times (1 - \frac{-2}{-4}) = 3 \text{ mA/V}$$