

## 九十八學年四技二專第三次聯合模擬考試 電機電子群電機類 專業科目 (二) 詳解

98-3-03-5

1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16	17	18	19	20	21	22	23	24	25
B	A	C	C	B	D	D	A	C	A	C	C	B	B	D	A	C	D	D	B	A	C	D	B	B
26	27	28	29	30	31	32	33	34	35	36	37	38	39	40	41	42	43	44	45	46	47	48	49	50
D	A	D	C	B	D	C	A	D	A	D	B	C	D	A	B	D	B	A	C	A	A	B	B	C


### 第一部份：電工機械

1. 
$$e = N \frac{\Delta\phi}{\Delta t} = N \frac{\Delta BA}{\Delta t} = 100 \times \frac{0.1 \times (0.1 \times 0.1)}{\frac{1}{600} \times \frac{1}{4}} = 4 \text{ V}$$
2. 
$$\frac{100}{200} = \frac{k \cdot \phi \cdot 50}{k \cdot 0.8\phi \cdot I'_a} \Rightarrow I'_a = 125 \text{ A}$$
4. 
$$a_{\text{疊}} = mp = 4, a_{\text{波}} = 2m = 2, \frac{a_{\text{疊}}}{a_{\text{波}}} = 2$$
6. 
$$100 \times (R_a + 5R_a) = 12 \Rightarrow R_a = 0.02 \Omega$$
  
$$R_s = 5R_a = 0.1 \Omega$$
8. 鐵損為固定損失
9. 
$$R'_2 = 0.01 + \frac{1}{100} = 0.02 \Omega$$
10. 
$$R' = 0.075 \times \frac{200}{50} = 0.3 \text{ Pu}, X' = 0.1 \times \frac{200}{50} = 0.4 \text{ Pu}$$
  
$$Z' = \sqrt{0.3^2 + 0.4^2} = 0.5 \text{ Pu}$$
11. 
$$\eta = \frac{8 \times 10 \text{ k} \times 1}{8 \times 10 \text{ k} \times 1 + 8 \times 0.24 + 24 \times 0.1} = \frac{80}{84.32} = 0.949$$
12. 
$$S_{\text{自}} = 100 \text{ k} \left(1 + \frac{1200}{400}\right) = 400 \text{ kVA}$$
14. 
$$n_s = \frac{120 \times 60}{6} = 1200 \text{ rpm}$$
  
$$s = \frac{n_s - n_r}{n_s} = \frac{1200 - 1000}{1200} = \frac{1}{6}, f_r = sf_s = \frac{1}{6} \times 60 = 10 \text{ Hz}$$


### 第二部份：電子學實習

19. N 型半導體多數載子為電子，少數載子為電洞
20.  $\because 12 \times \frac{100 \text{ k}}{100 \text{ k} + 5 \text{ k}} > 6 \text{ V}, D_2 \text{ ON}, D_1 \text{ OFF}, V_o = 6 \text{ V}$
21. 
$$I_s = 0 + 6 \text{ m} = \frac{12 - 6}{R_s} \Rightarrow R_s = 1 \text{ k}\Omega$$
22. 
$$V_m = 110\sqrt{2} \text{ V}, V_{r(p-p)} = \frac{V_m}{R_L C \times f_r}$$
  
$$= \frac{110\sqrt{2}}{1 \text{ k}\Omega \times 1000 \mu\text{F} \times 60 \text{ Hz}} = \frac{11\sqrt{2}}{6} \Rightarrow V_{r(m)} = \frac{V_{r(p-p)}}{2} = 1.3$$

23.

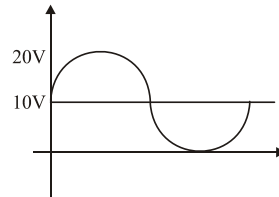

24. 電晶體在主動區時，BE 接面順偏，CB 接面逆偏
  25. 採近似解法，
$$V_B = -10 \cdot \frac{10 \text{ k}}{10 \text{ k} + 40 \text{ k}} = -2 \text{ V}$$
  
$$I_E = \frac{2 - 0.7}{1 \text{ k}} = 1.3 \text{ mA} \cong I_C$$
  26. 
$$I_E = \frac{10 - 0.7}{1 \text{ k} + \frac{100 \text{ k}}{1 + 100}} \cong \frac{9.3}{2 \text{ k}} = 4.65 \text{ mA} \cong I_C$$
  
$$V_{EC} = 20 - 4.65 \text{ m} \cdot (1 \text{ k} + 2 \text{ k}) = 6.05 \text{ V}$$
  
$$V_{CE} = -V_{EC} = -6.05 \text{ V}$$
  27. 此電晶體工作於飽和區，因此  $A_V = 0$
  28. 耦合電容、旁路電容影響低頻響應，極點電容、雜散電容影響高頻響應
  29. 電壓增益近似於 1
  31.  $\because I_G = 0, \therefore V_{GS} = V_{DS}, I_D = K(V_{GS} - V_T)^2$   
$$\frac{8 - V_{DS}}{1 \text{ k} + 1 \text{ k}} = 0.5 \text{ m}(V_{DS} - 2)^2 \Rightarrow V_{DS}^2 - 3V_{DS} - 4 = 0$$
  
$$\Rightarrow V_{DS} = 4, -1(\text{不合}), I_D = \frac{8 - 4}{2 \text{ k}} = 2 \text{ mA}$$
  32. 
$$g_m = \frac{2I_{DSS}}{|V_P|} \left(1 - \frac{V_{GS}}{V_P}\right) = \frac{2 \cdot 12 \text{ m}}{4} \left(1 - \frac{-2}{-4}\right) = 3 \text{ mS}$$
  33. 
$$10 \text{ k} \cdot i = R \cdot 8i \Rightarrow R = \frac{5}{4} \text{ k}\Omega$$
  34. 
$$V_o = 6 - 2 \text{ m} \times 2 \text{ k} + 3 = 5 \text{ V}$$
- ### 第三部份：基本電學實習
35. 
$$R_A = 3R_Y = 3 \times 4 \Omega = 12 \Omega$$
  
$$R_{AB} = [(12 // 12) + (12 // 6)] // 12$$
  
$$= 10 // 12 = \frac{60}{11} \Omega$$
  36. 
$$I = \frac{100}{100} + \frac{100}{50} + \frac{100}{25} = 7 \text{ A} > 5 \text{ A}$$
  
 $\therefore$  保險絲燒斷， $I = 0 \text{ A}$

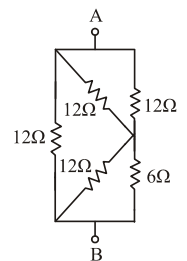


37.  $20 = 2R + 4 \times (R + 2) \Rightarrow R = 2 \Omega$

38. 因  $1 \Omega$  與  $6V$  並聯，可忽略  $1 \Omega$

$$V_a = \frac{7+3}{\frac{1}{2} + \frac{1}{2}} = 10V$$


$$I = \frac{10}{2} = 5A$$

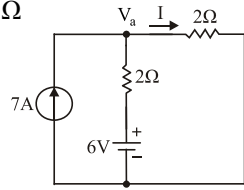

39.  $R \downarrow, I \uparrow, P \uparrow, H \uparrow$

40. 左右兩邊取戴維寧等效電路

$$I = \frac{9-2}{3+2+2} = 1A$$

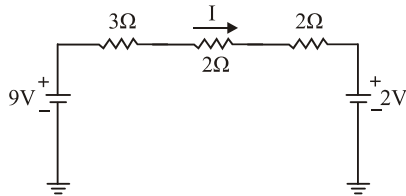

46.  $I_1 = \frac{100 \angle 0^\circ}{6 + j8} = 6 - j8$ ,  $I_2 = \frac{100 \angle 0^\circ}{8 - j6} = 8 + j6$

$$I = I_1 + I_2 = 14 - j2 = 10\sqrt{2} \angle 0^\circ$$

47.  $R_{\text{串}} = \frac{30^2 + 30^2}{30} = 60 \Omega$ ,  $X_{\text{串}} = \frac{30^2 + 30^2}{30} = 60 \Omega$

$$Z'_{\text{串}} = 60 + j(60 \times 2) = 60 + j120 \Omega$$

48.  $T_s = \frac{1}{f} = 1 \text{ mS}$ ,  $T_1 = 1 \text{ mS} \times \frac{90}{360} = 0.25 \text{ mS}$

50.  $\bar{I} = \frac{\bar{E}}{8 + j6} = \frac{100 \angle 0^\circ}{10 \angle 37^\circ} = 10 \angle -37^\circ A$

$$P_R = I^2 R = 10^2 \times 8 = 800 W$$