

103 學年度四技二專第一次聯合模擬考試 電機與電子群 專業科目(一) 詳解

103-1-03-4、103-1-04-4

1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16	17	18	19	20	21	22	23	24	25
C	B	A	A	D	C	B	B	D	C	B	B	B	C	C	C	A	D	A	C	A	B	B	D	C
26	27	28	29	30	31	32	33	34	35	36	37	38	39	40	41	42	43	44	45	46	47	48	49	50
B	C	C	C	D	C	C	D	C	B	B	A	C	C	C	A	C	D	D	C	A	B	B	C	C


第一部分：基本電學

1. 由圖(一)-a 得知 $R_1(\Omega) = R_2(\Omega)$

故圖(一)-b 的 $I_T = \frac{3E}{5} A$





流過圖(一)-b 的 R_2 電流 $= \frac{E}{5} A$ ，所以 $V_2 = \frac{1}{5} E V$

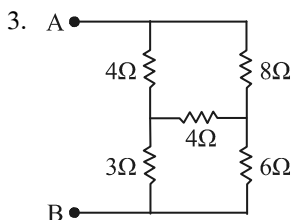2. $552 \text{ 卡} = V \times 2 \times 10 \times 0.24 \Rightarrow V = 115 V$



故 $R_{AB} = (4 // 8) + 2 = \frac{14}{3} \Omega$

4. 原圖 \Rightarrow

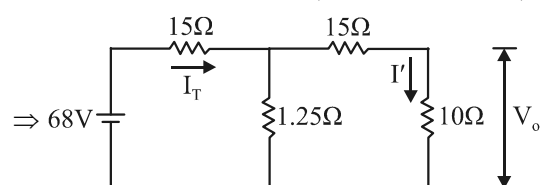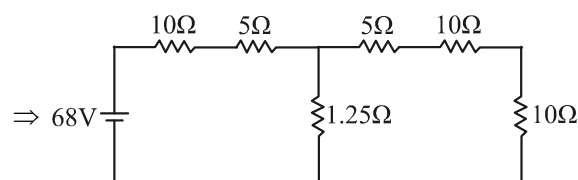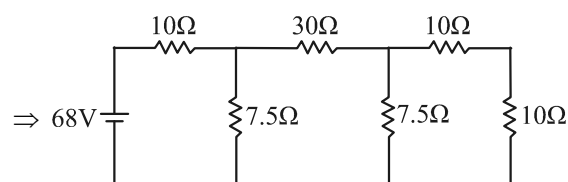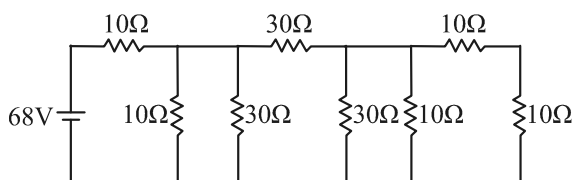


$I_T = \frac{68}{15 + (25 // 1.25)} = 4.2 A$ ， $I' = 4.2 \times \frac{1}{21} = 0.2 A$

故 $V_o = 0.2 \times 10 = 2 V$

5. $I_T = \frac{60}{30} = 2 A$ ， $I = -2 \times \frac{20}{30 + 20} = -0.8 A$

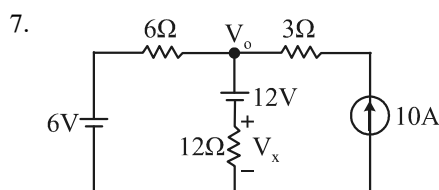6. 使用諾頓等效模型分析， $I = \frac{120}{10} + 8 + \frac{100}{5 + 5} = 30 A$



$\frac{V_o - 6}{6} + \frac{V_o - 12}{12} = 10$ ， $2V_o - 12 + V_o - 12 = 120$

$3V_o = 144$ ， $V_o = 48 V$


故 $V_x = V_o - 12 = 48 - 12 = 36 V$

8. 達因為力學單位

9. $\frac{E}{R} = \frac{10}{4} = I = 2.5 = \frac{Q}{t} = \frac{n \times 1.602 \times 10^{-19}}{2 \times 60}$


$\Rightarrow n = 1.875 \times 10^{21}$ 個電子

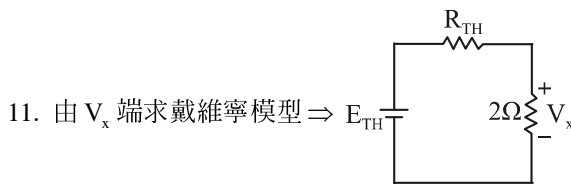10. $\frac{R_{甲}}{R_{乙}} = \frac{3S}{2L} = \frac{2}{3}$ ，因 $I = \frac{V}{R}$ ，故 $\frac{V_{甲}}{V_{乙}} = \frac{2}{3}$



$E_{TH} = 16 \times \frac{3}{5} + 8 = \frac{88}{5} V$ ， $R_{TH} = 2 // 3 = \frac{6}{5}$

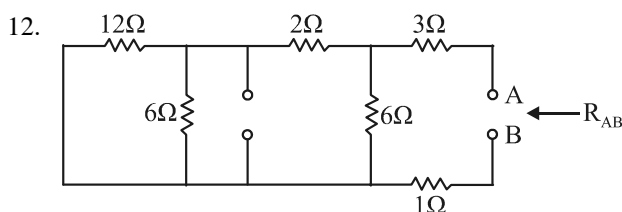故 $V_x = \frac{88}{5} \times \frac{2}{\frac{6}{5} + 2} = \frac{88}{5} \times \frac{5}{16} = 11 V$



$R_{AB} = R_L = \{[(12 // 6) + 2] // 6\} + 3 + 1 = 7 \Omega$


13. 使用密爾門定理, $E_{TH} = \frac{\frac{20}{2} + \frac{32}{4} + \frac{-24}{8}}{\frac{1}{2} + \frac{1}{4} + \frac{1}{8} + \frac{1}{16}} = 16 \text{ V}$

14. 電路為惠斯登電橋

故 $R_{TH} = (4+6+5+10) // (5+2.5+5) = \frac{25}{3} \text{ k}\Omega$


則 $I = \frac{25}{\frac{25}{3}} = 3 \text{ mA}$

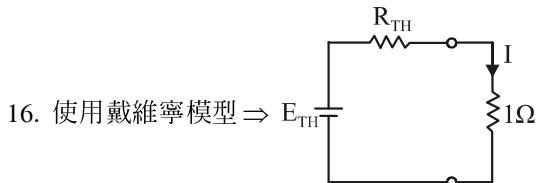15. 使用重疊定理 $I_x = (-9 \times \frac{4}{4+2}) + (\frac{-12}{4+2}) = -8 \text{ A}$



16. 使用戴維寧模型 $\Rightarrow E_{TH} = 48 - 36 = 12 \text{ V}$, $R_{TH} = (3 // 6) + (6 // 6) = 5 \Omega$

故 $I = \frac{12}{5+1} = 2 \text{ A}$

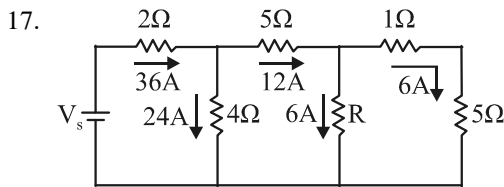

17. 故 $R = \frac{6(1+5)}{6} = 6 \Omega$

18. 以 L_1 迴路依 KCL $\Rightarrow (12-6) = 6I_1 + 6(I_1 + I_2)$
 $= 12I_1 + 6I_2 = 6 \Rightarrow 2I_1 + I_2 = 1$, 故 $x = 2$, $y = 1$
 則 $x + y = 3$


19. $R_2 = R_1[1 + \alpha_1(50)] = 20 \text{ k}\Omega \times [1 + (0.006 \times 50)] = 26 \text{ k}\Omega$

故 $I = \frac{100}{26 \text{ k}\Omega} \div 3.85 \text{ mA}$

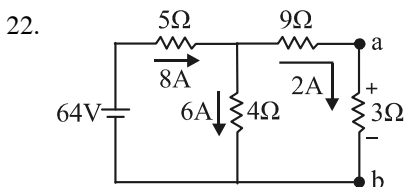21. 使用重疊定理, 求出流經 4Ω 的電流

$= [10 \times \frac{6}{4+6}] - [5 \times \frac{6}{4+6}] - [\frac{10}{4+6}] = 2 \text{ A}$

則 $P_{4\Omega} = 2^2 \times 4 = 16 \text{ W}$



22. 故 $V_{ab} = V_{3\Omega} = 2 \times 3 = 6 \text{ V}$


23.
$$\begin{cases} R_A + R_B = \frac{6}{3} = 2 \Omega \\ R_B + R_C = \frac{7.5}{3} = 2.5 \Omega \\ R_A + R_C = \frac{6.75}{2.5} = 2.7 \Omega \end{cases} \Rightarrow \begin{cases} R_A = 1.1 \Omega \\ R_B = 0.9 \Omega \\ R_C = 1.6 \Omega \end{cases}$$

24. $E_{TH} = (40 \times \frac{1}{3}) + (40 \times \frac{2}{3}) + (40 \times \frac{1}{2}) = 60 \text{ V}$

$R_{TH} = (6 // 3) + (4 // 4) = 4 \Omega$

故 $R = R_{TH} = 4 \Omega$ 時有最大功率

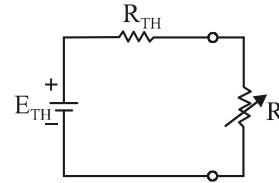則 $P_{max} = \frac{30^2}{4} = 225 \text{ W}$



25. 使用重疊得知 3 A 並聯的 4Ω 的電流為 $3 \text{ A} \uparrow$

故 $V_{4\Omega} = (-3) \times 4 = -12 \text{ V}$

則電源源 3 A 的功率為 $= 3 \times (-12) = -36 \text{ W}$

第二部分：電子學

26. $V(\frac{1}{600}) = 100\sqrt{2} \sin(314 \times \frac{1}{600} \times \frac{180^\circ}{\pi} + 15^\circ)$
 $= 100\sqrt{2} \sin 45^\circ = 100\sqrt{2} \times \frac{1}{\sqrt{2}} = 100 \text{ V}$

27. 在 P 型半導體中, 電子被稱為少數載子

28. 設 D_1 , OFF/ D_2 , ON

$\frac{6 - 0.7 - V}{5 \text{ k}} = \frac{V - (-6)}{10 \text{ k}}$


$\Rightarrow 10.6 - 2 \text{ V} = V + 6$

$\Rightarrow 3 \text{ V} = 4.6$

$\Rightarrow V = 1.533 \text{ V}$

故假設成立

D_1 , OFF/ D_2 , ON

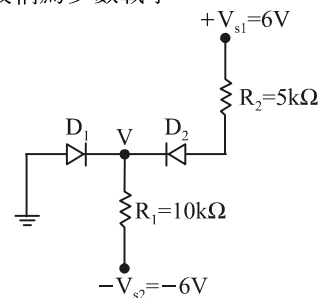

29. 變壓器 2 次側 $V = 10\sqrt{2}$, $V_m = 20$

故 $V_{c2} = 2V_m = 40$, $V_{c4} = 2V_m = 40$

則 $V_o = V_{c2} + V_{c4} = 80 \text{ V}$

30. 電源端部分為 $+15 \text{ V} \sim -5 \text{ V}$

並聯截波部分為 $+7 \text{ V} \geq V_o \geq -7 \text{ V}$

綜合上面兩部分分析 \Rightarrow 得 $+7 \text{ V} \geq V_o \geq -5 \text{ V}$

31. 分析時先拿掉 Zener, $I_B = \frac{2.7 - 0.7}{100 \text{ k}} = 20 \mu\text{A}$

$I_{C(sat)} = \frac{8.2 - 0.2}{1.6 \text{ k}} = 5 \text{ mA}$, 因 $\beta I_B < I_{C(sat)}$

\Rightarrow 故 BJT 工作在工作區, 故 $I_C = 2 \text{ mA}$

$V_o = V_{CE} = 8.2 - (1.6 \times 2) = 5 \text{ V}$ 因 $V_o = 5 \text{ V} > V_z$

\Rightarrow 故 Zener 崩潰工作所以 $V_o = V_z = 4 \text{ V}$

33. 稽納二極的逆向崩潰電壓與摻雜濃度成反比

34. $V_{r.m.s} = \sqrt{\frac{(\frac{20}{\sqrt{3}})^2 \times 2}{4}} = 8.16 \text{ V}$

36. 射極隨耦器為集極接地式(CC)放大器

37. 價電子要獲得足夠的熱量, 才能使共價鍵斷裂, 變


為自由電子

38. 由圖(二十五)-a 中得知 $V_z = 5.6 \text{ V}$

$$r_z = \frac{\Delta V}{\Delta I} = \frac{6 - 5.6}{8 \text{ mA}} = 50 \Omega$$

由圖(二十五)-b 中得知 $14 \times \frac{100}{100 + 100} = 7 \text{ V} > V_z$

Zener 崩潰工作

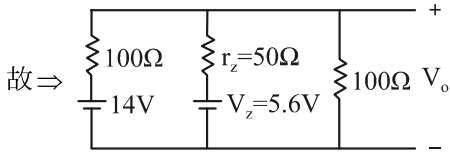

$$V_o = \frac{\frac{14}{\frac{1}{100} + \frac{1}{50}} + \frac{5.6}{1}}{\frac{1}{100} + \frac{1}{50} + \frac{1}{100}} = 6.3 \text{ V}$$

42. 變壓器 2 次側為 10 V，而該電路為半波整流濾波電路，所以輸出為 $V_o(\text{dc}) \doteq V_m = 10\sqrt{2} = 14.14 \text{ V}$

43. 漣波因數愈小，表示濾波效果愈好

44. 電流增益最大的為共集極(CC)

45. 偏壓與控制輸出增益的倍數無關

$$46. I_{C2} = \frac{V_{CC} - V_{C2}}{0.8 \text{ k}} = \frac{12 - 8}{0.8 \text{ k}} = 5 \text{ mA} = I_{E2}$$

$$I_{B2} = \frac{I_{E2}}{1 + \beta_2} = \frac{5 \text{ mA}}{101} = 50 \mu\text{A}$$

$$I_{RC1} = \frac{V_{CC} - V_{C1}}{12 \text{ k}} = \frac{12 - 6}{12 \text{ k}} = 0.5 \text{ mA}$$

$$I_{RC1} = I_{C1} + I_{B2} \Rightarrow I_{C1} = I_{RC1} - I_{B2} = 0.5 \text{ mA} - 50 \mu = 450 \mu\text{A}$$

$$I_{B1} = \frac{I_{C1}}{\beta_1} = \frac{450 \mu}{50} = 9 \mu\text{A}$$

$$47. I_E \cong I_C = \frac{V_{CC} - V_{EB}}{3 \text{ k}} = \frac{12 - 0.7}{3 \text{ k}} = \frac{11.3}{3 \text{ k}}$$

$$V_{CC} - V_{EC} - V_{SS} = I_E(R_C + R_E)$$

$$\Rightarrow \frac{12 - 0.3 - (-12)}{\frac{11.3}{3 \text{ k}}} = 3 \text{ k} + R_C \Rightarrow R_C \doteq 3.3 \text{ k}\Omega$$

48. 工作點 Q_1 移動到 Q_2 代表 $I_C \uparrow$

$$I_C = \beta I_B = \beta \left(\frac{V_{CC} - V_{BE}}{R_B} \right)$$


故 $I_C \uparrow$ 時 $R_B \downarrow$

$$49. I_B = \frac{5 - 0.7}{50 \text{ k}\Omega} = 0.086 \text{ mA}$$


$$I_C = \beta I_B = 4.3 \text{ mA}$$

$$V_C = 10 - 4.3 = 5.7 \text{ V}$$

$$V_{CE} = V_C - V_E = 5.7 \text{ V}$$

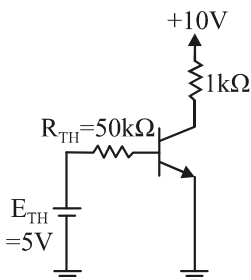

50.

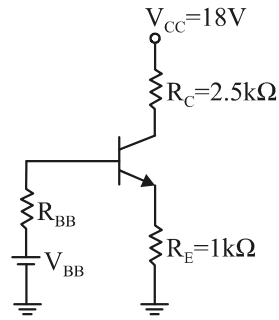

$$R_{BB} = 10 \text{ k}\Omega // 10 \text{ k}\Omega = 5 \text{ k}\Omega$$

$$V_{BB} = 18 \times \frac{10 \text{ k}\Omega}{10 \text{ k}\Omega + 10 \text{ k}\Omega} = 9 \text{ V}$$

$$I_{C(\text{sat})} = \frac{18 - 0.2}{2.5 \text{ k} + 1 \text{ k}} = 5.086 \text{ mA}$$

$$V_{BB} = I_B R_{BB} + (1 + \beta) I_B R_E + V_{BE}$$

$$\Rightarrow 9 - 0.7 = I_B \times 5 \text{ k} + 95 \times I_B \times 1 \text{ k}$$

$$\Rightarrow I_B = \frac{8.3}{100 \text{ k}} = 0.083 \text{ mA}$$

因 $\beta I_B > I_{C(\text{sat})} \Rightarrow$ 故工作在飽和區

$$\begin{cases} 9 = I_B \times 5 \text{ k} + 0.8 + (I_B + I_C) \times 1 \text{ k} \\ 18 = I_C \times 2.5 \text{ k} + 0.2 + (I_B + I_C) \times 1 \text{ k} \end{cases}$$

$$\Rightarrow \begin{cases} I_B = 0.545 \text{ mA} \\ I_C = 4.93 \text{ mA} \end{cases}$$