


103 學年度四技二專第三次聯合模擬考試 電機與電子群 專業科目(一) 詳解

103-3-03-4、103-3-04-4

1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16	17	18	19	20	21	22	23	24	25
C	B	C	A	C	D	B	B	C	D	C	A	B	D	A	C	B	A	B	D	A	B	B	D	A
26	27	28	29	30	31	32	33	34	35	36	37	38	39	40	41	42	43	44	45	46	47	48	49	50
A	D	B	D	A	D	C	C	B	B	D	C	A	D	A	B	C	D	C	B	A	A	C	B	D


第一部分：基本電學

- $W = FS = Pt = IVt$, $\therefore \eta = \frac{W_o}{W_i} = \frac{FS}{IVt}$
 $\therefore I = \frac{FS}{Vt\eta} = \frac{200 \times 10}{100 \times 5 \times 0.8} = 5 \text{ A}$
- $\frac{R_{甲}}{R_{乙}} = \frac{l_{甲}}{l_{乙}} \times \frac{A_{乙}}{A_{甲}} = \frac{L}{4L} \times \frac{2S}{S} = \frac{1}{2}$
 又 $V = IR$, $\therefore V \propto R$, $\frac{V_{乙}}{V_{甲}} = \frac{2}{1}$
- 黃、黑、金、金 $\Rightarrow 40 \times 10^{-1} \pm 5\% = 4 \Omega \pm 5\%$
 $R_{\min} = 4 \Omega \times (1 - 5\%) = 3.8 \Omega$
 $\therefore P_{\max} = \frac{V^2}{R} = \frac{10^2}{3.8} = 26.3 \text{ W}$
- $I_T = \frac{6}{\frac{R}{3}} = \frac{18}{R} \text{ A}$, $V_C = I_T \times \frac{R}{2} = \frac{18}{R} \times \frac{R}{2} = 9 \text{ V}$
 $V_A = I_T \times R = \frac{18}{R} \times R = 18 \text{ V}$
 $E = V_A + V_B + V_C = 6 + 9 + 18 = 33 \text{ V}$
- 合併同電位點如右圖
 $R_T = \frac{10}{5} + R_6 = 2 + 10 = 12 \Omega$
 $I_T = \frac{E}{R_T} = \frac{60}{12} = 5 \text{ A}$
 $I_{R_3} = \frac{I_T}{5} = \frac{5}{5} = 1 \text{ A}$
 $P_{R_{3\Omega}} = I^2 R = 1^2 \times 10 = 10 \text{ W}$
- $\therefore V_1 = 0.5 \text{ E}$, $\therefore R_1 = R_2$
 $R_T = [(2R_2 // R_2) + R_1] = [(2R_2 // R_2) + R_2] = \frac{5}{3} R_2 \Omega$
 $I_T = \frac{E}{R_T} = \frac{E}{\frac{5}{3} R_2} = \frac{3E}{5R_2} \text{ A}$
 $I_2 = I_T \times \frac{3E}{5R_2} \times \frac{R_2}{R_2 + 2R_2} = \frac{E}{5R_2} \text{ A}$
 $\therefore V_2 = I_2 \times R_2 = \frac{E}{5R_2} \times R_2 = \frac{1}{5} E$
- $R_T = 1 + (3 // 9) + (5 // 15) + 2 = 1 + 6 + 2 = 9 \Omega$

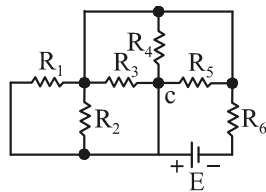

$$I_T = \frac{E}{R_T} = \frac{108}{9} = 12 \text{ A} , I_1 = I_T \times \frac{3}{9+3} = 3 \text{ A}$$

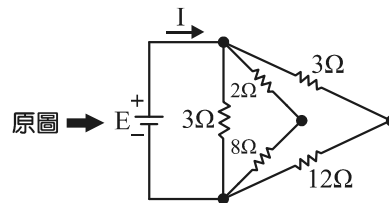- 因 $12 \times 2 = 3 \times 8$, 電橋達平衡 , 10Ω 電阻可移除
 $I_{10\Omega} = 0 \text{ A}$, $P_{10\Omega} = 0 \text{ W}$
 $R_T = 3 // (2+8) // (3+12) = 3 // 6 = 2 \Omega$
 $\therefore E = I \times R_T = 2 \times 6 = 12 \text{ V}$



- $$\begin{cases} (3+12)I_1 - 12I_2 = 12 \\ I_2 = -6 \end{cases} , I_1 = -4 \text{ A}$$

 化簡得 $I = I_1 - I_2 = -4 - (-6) = 2 \text{ A}$

$$10. V_a = \frac{9+0+\frac{12}{2+2}}{\frac{1}{4}+\frac{1}{2+2}} = 24 \text{ V}$$

$$I_x = \frac{E - V_a}{2+2} = \frac{12-24}{4} = -3 \text{ A}$$

- 球內之電場強度為 0 , 球表面之電場強度最強

$$12. \therefore W = \frac{1}{2} CV^2 , \text{ 並聯} \Rightarrow V \text{ 相同} , \therefore W \propto C$$

$$W_1 : W_2 : W_3 = 2 : 3 : 6$$

$$13. H = \frac{NI}{\ell} = \frac{100 \times 1}{1} = 1 \times 10^2 \text{ 牛頓/韋伯}$$

$$B = \mu H = 4\pi \times 10^{-7} \times 1 \times 10^2 = 4\pi \times 10^{-5} \text{ 韋伯/平方公尺}$$

$$\phi = A \times B = \pi \times (0.05)^2 \times 4\pi \times 10^{-5} \approx 9.87 \times 10^{-7} \text{ 韋伯}$$

$$14. L = N \frac{\Delta \phi}{\Delta I} = N \frac{\phi}{I} = 500 \times \frac{2 \times 10^6 \times 10^{-8}}{4} = 2.5 \text{ H}$$

(注意單位)

$$\therefore L = \frac{\mu AN^2}{\ell} = \frac{N^2}{R} , \therefore L \propto N^2$$

$$\therefore L' = L \left(\frac{N'}{N}\right)^2 = 2.5 \times \left(\frac{750}{500}\right)^2 = 5.625 \text{ H}$$


$$15. H = \frac{I}{2\pi r} , \therefore H \propto \frac{1}{r} , \frac{H_1}{H} = \frac{8}{4} = 2$$

- 開關閉合很久達穩態後 , 電感器視為短路 , 電容器視為斷路 , 如下圖所示 $8 \text{ k}\Omega$ 電阻被旁路

$$\therefore I_C = 0 \text{ mA}$$

$$\therefore R_T = R_1 + R_2 = 10 \text{ k} + 4 \text{ k} = 14 \text{ k}\Omega$$
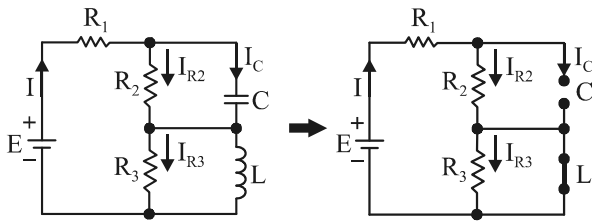
$$\therefore I = \frac{V}{R_T} = \frac{28}{14 \text{ k}} = 2 \text{ mA} = I_{R_2}$$



17. 先求 $20 \mu\text{F}$ 兩端之戴維寧等效電路

$$E_{\text{TH}} = V_{60\text{k}} = 90 \times \frac{60 \text{ k}}{30 \text{ k} + 60 \text{ k}} = 60 \text{ V}$$

$$R_{\text{TH}} = 10 \text{ k} + (30 \text{ k} // 60 \text{ k}) = 30 \text{ k}\Omega$$

$$\therefore i_C(t) = \frac{60}{30 \text{ k}} \times e^{-\frac{0.6}{30\text{k} \times 20\mu}} = 2e^{-t} \text{ mA}$$

18. $v_R(0) = -(v_R + E_2) = -(60 + 30) = -90 \text{ V}$

$$\tau = 500 \times 10 \mu = 5 \text{ ms}$$

$$v_R(t) = v_R(0) \times e^{-\frac{t}{\tau}} = -90 \times e^{-\frac{t}{5 \times 10^{-3}}} = -90 \times e^{-200t} \text{ 伏特}$$

19. $V_m = \sqrt{2} V_{\text{rms}} = 100\sqrt{2} \text{ V}$, $V_{\text{av}} = \frac{V_m}{\pi} = \frac{100\sqrt{2}}{\pi} = 45 \text{ V}$

20. $\theta = \omega t = 2\pi f t$, $\therefore 18^\circ = 2\pi \times 100 \times \frac{180^\circ}{\pi} \times t$

$$\therefore t = 0.5 \text{ ms}$$

21. $\bar{Z} = \frac{\bar{E}}{\bar{I}} = \frac{100}{10} = 10 \Omega = R + jX_L = 8 + jX_L$

$$\text{得 } X_L = \sqrt{10^2 - 8^2} = 6 \Omega$$

$$\text{得 } L = \frac{6}{2 \times 3.14 \times 60} \cong 16 \text{ mH}$$

因此 $L \geq 16 \text{ mH}$

22. $\bar{Z}_1 = R + j(X_L - X_C) = 40 + j(30 - 60)$
 $= 40 - j30 = 50 \angle -37^\circ \Omega$

$$\text{當 } f' = 2f \Rightarrow X'_L = 2X_L = 60 \Omega, X'_C = \frac{1}{2}X_C = 30 \Omega$$

$$\therefore \bar{Z}_2 = 40 + j(60 - 30) = 40 + j30 = 50 \angle 37^\circ \Omega$$

$$\therefore Z_1 = Z_2 \Rightarrow I_2 = I_1, \text{ 故爲 } 1 \text{ 倍, 但 } \bar{Z}_1 \neq \bar{Z}_2$$

23. $I_R = \frac{P}{E} = \frac{3.6 \text{ k}}{120} = 30 \text{ A}$

$$I_X = \sqrt{I^2 - I_R^2} = \sqrt{50^2 - 30^2} = 40 \text{ A}$$

24. $P_{\text{max}} = P + S = EI(\cos\theta + 1) = \frac{110}{\sqrt{2}} \times \frac{5}{\sqrt{2}} (\cos 30^\circ + 1)$
 $= 513 \text{ W}$

25. $p\left(\frac{1}{100}\right) = 1000 - 2000 \cos\left(628 \times \frac{1}{100} \times \frac{180^\circ}{\pi} + 60^\circ\right)$
 $= 1000 - 2000 \cos 60^\circ = 0 \text{ W}$

第二部分：電子學

26. $V(t) = 50\sqrt{2} + 60 \sin t - 60 \cos(t - 30^\circ) + 80 \sin 3t$

$$= 50\sqrt{2} + 60 \sin t - 60 \sin(t + 60^\circ) + 80 \sin 3t$$

$$= 50\sqrt{2} + 60 \sin(t - 60^\circ) + 80 \sin 3t$$

$$V_{\text{rms}} = \left[(50\sqrt{2})^2 + \left(\frac{60}{\sqrt{2}}\right)^2 + \left(\frac{80}{\sqrt{2}}\right)^2 \right]^{\frac{1}{2}} = \sqrt{10000} = 100 \text{ V}$$

27. (A) 逆向漏電流隨溫度上升而上升
 (B) 擴散電容只有在順向偏壓時才存在
 (C) 電表的探針和二極體的內建電位會互相抵消，因此無法直接測得內建電位

28. $V_i > 5.7 \text{ V}$, D 導通, $V_o = 5.7 \text{ V}$

$$V_i < 5.7 \text{ V}, \text{ D 截止, } V_o = V_i$$

29. D_1 截止、 D_2 導通, $I = 0$

$$\text{因此 } \frac{5 - V_o}{5 \text{ k}} = \frac{V_o - (-5)}{2.5 \text{ k}}, \text{ 故 } V_o = -\frac{5}{3} \text{ V}$$

30. 二次側電壓 $V_2 = \frac{120}{5} = 24 \text{ V}$

$$\text{負載峰值電壓 } V_p = 24\sqrt{2} - 0.7 = 34 - 0.7 = 33.3 \text{ V}$$

$$\text{負載 } R_L \text{ 的直流電壓 } V_{\text{dc}} \doteq \frac{V_p}{\pi} = \frac{33.3}{\pi} = 10.6 \text{ V}$$

31. 二次側電壓 $V_2 = \frac{120}{5} = 24 \text{ V}$

$$\text{二次側峰值電壓 } V_p = 24\sqrt{2} = 34 \text{ V}$$

$$\text{負載電流 } I_L = \frac{V_p}{R_L} = \frac{34}{5 \text{ k}} = 6.8 \text{ mA}$$

$$V_{r(P-P)} = \frac{I_L}{2f_1 \times C} = \frac{6.8 \times 10^{-3}}{2 \times 60 \times C} = 0.566 \text{ V}$$

$$C \doteq 100 \mu\text{F}$$

33. (A) 在飽和區時, I_C 隨 V_{CE} 增加而增加; 在主動區時, I_C 才是幾乎和 V_{CE} 無關

(B) 在截止區時, I_B 趨近於 0, V_{CE} 不必一定趨近於 0

(D) 電流增益 $I_C = \beta_{\text{dc}} I_B$ 僅在主動區成立

34. $I_C \doteq I_E = \frac{V_{\text{CC}} - V_{\text{BE}}}{R_C + \frac{R_B}{\beta_{\text{dc}}}} \dots\dots \textcircled{1}$

$$\text{當 } \beta_{\text{dc}} = 100 \text{ 時, } I_C = 4.77 \text{ mA}$$

$$\text{由 } \textcircled{1} \text{ 式可得 } R_B = 200 \text{ k}\Omega$$

$$\text{當 } \beta_{\text{dc}} = 300 \text{ 時, 由 } \textcircled{1} \text{ 式可得 } I_C \doteq 8.58 \text{ mA}$$

35. $V_B = \frac{V_{\text{CC}} \times R_2}{R_1 + R_2} = -1.8 \text{ V}$

$$V_E = V_B + V_{\text{EB}} = -1.1 \text{ V}$$

$$I_C = I_E = \frac{-V_E}{R_E} = 1.1 \text{ mA}$$

$$V_C = V_{\text{CC}} + I_C R_C = -6.04 \text{ V}$$

$$V_{\text{CE}} = V_C - V_E = -4.94 \text{ V}$$

36. 功率增益: $\text{CE} > \text{CB} > \text{CC}$

37. $V_{BQ} = \frac{10 \times 2.2 \text{ k}}{10 \text{ k} + 2.2 \text{ k}} = 1.8 \text{ V}$, $V_{EQ} = 1.8 - 0.7 = 1.1 \text{ V}$

$I_{EQ} \doteq \frac{1.1}{180 + 820} = 1.1 \text{ mA}$, $r_c = \frac{25 \text{ mV}}{1.1 \text{ mA}} = 22.7 \Omega$

$Z_{in(\text{base})} = (1 + 200)(180 + 22.7) = 40.7 \text{ k}\Omega$

$Z_{in(\text{stage})} = 10 \text{ k} \parallel 2.2 \text{ k} \parallel 40.7 \text{ k} = 1.72 \text{ k}\Omega$

$V_{in} = 50 \text{ mV} \times \frac{1.72 \text{ k}}{600 + 1.72 \text{ k}} = 37 \text{ mV}$

$Z_{out(\text{collector})} = 3.6 \text{ k} \parallel 10 \text{ k} = 2.65 \text{ k}\Omega$

$V_{out} = -37 \text{ mV} \times \frac{2.65 \text{ k}}{180 + 22.7} = -485 \text{ mV}$

38. $V_{BQ} = 30 \times \frac{10 \text{ k}}{10 \text{ k} + 10 \text{ k}} = 15 \text{ V}$

$I_{EQ} \doteq \frac{15}{100} = 150 \text{ mA}$

$r_c = \frac{25 \text{ mV}}{150 \text{ mA}} = 0.167 \Omega$

$Z_{out} = 100 \parallel [0.167 + \frac{(10 \text{ k} \parallel 10 \text{ k} \parallel 600)}{300}] = 1.91 \Omega$

40. $\frac{V_o}{V_{i2}} = 240 \times \frac{8.2 \text{ k}}{5.1 \text{ k} + 8.2 \text{ k}} = 148$

$\frac{V_{i2}}{V_{i1}} = \frac{1 \times 26}{12 + 26} = 0.68$

$\frac{V_{i1}}{V_{in}} = \frac{10 \text{ k}}{1 \text{ k} + 10 \text{ k}} = 0.91$

$\frac{V_o}{V_{in}} = (\frac{V_o}{V_{i2}})(\frac{V_{i2}}{V_{i1}})(\frac{V_{i1}}{V_{in}}) = 91.6$

41. Q_1 為 CB 放大器 , $\frac{V_o}{V_x} = \frac{\alpha R_c}{r_c} = g_m R_c$

Q_2 為 CE 放大器 , $\frac{V_x}{V_{in}} = -1$

$\frac{V_o}{V_{in}} = (\frac{V_o}{V_x})(\frac{V_x}{V_{in}}) = -g_m R_c$

42. MOSFET 操作速度較 BJT 慢

43. 假設 Q 操作在飽和區 , 則 $I_D = I_{DSS}(1 - \frac{V_{GS}}{V_p})^2$

即 $2 \text{ mA} = 8 \text{ mA}(1 + \frac{V_{GS}}{4})^2$, 可得 $V_{GS} = -2 \text{ V}$

$\therefore V_G = 0$, $\therefore V_S = 2 \text{ V}$, $V_D = V_S + V_{DS} = 8 \text{ V}$

$V_{GD} = V_G - V_D = 0 - 8 = -8 \text{ V} < -4 = V_p$

(Q 確實操作在飽和區)

$R_S = \frac{V_S}{I_D} = \frac{2}{2 \text{ m}} = 1 \text{ k}\Omega$

$R_D = \frac{10 - V_D}{I_D} = \frac{10 - 8}{2 \text{ m}} = 1 \text{ k}\Omega$

44. Q_1 必操作在飽和區 , 且 $I_{G1} = I_{G2} = 0$

$V_{G1} = V_{G2} = V_{GS1} = V_{GS2} = V_{D1}$, 因此

$I_{D1} = \frac{10 - V_{D1}}{15 \text{ k}} \dots\dots\dots \textcircled{1}$

$I_{D1} = 0.1 \text{ m}(V_{D1} - 2)^2 \dots\dots\dots \textcircled{2}$

由①②式可解得 $V_{D1} = 4 \text{ V}$, $I_{D1} = 0.4 \text{ mA}$

$V_{GS2} = V_{D1} = 4 \text{ V}$, 假設 Q_2 操作在飽和區 , 因 Q_1 與

Q_2 特性相同 , 所以 $I_{D2} = 0.1 \text{ m}(4 - 2)^2 = 0.4 \text{ mA}$

$V_{D2} = 10 - 0.4 \text{ m} \times 10 \text{ k} = 6 \text{ V}$

$V_{GD2} = V_{G2} - V_{D2} = 4 - 6 = -2 \text{ V} < 2 = V_t$

(Q_2 確實操作在飽和區)

46. $g_{m0} = \frac{2I_{DSS}}{|V_p|} = 5 \text{ mS}$

$g_m = g_{m0}(1 - \frac{V_{GSQ}}{V_p}) = 2.25 \text{ mS}$

$V_o = g_m R_D V_i = 324 \text{ mV}$

47. $g_m = 2K(V_{GSQ} - V_t) = 1.63 \text{ mS}$

$\frac{V_o}{V_i} \doteq -g_m(r_o \parallel R_D \parallel R_G) = -3.2$

48. (A) 當負載電阻等於 $10 \text{ k}\Omega$ 時 , 此運算放大器的輸出電壓最大峰對峰值(MPP)約於 27 V , 因此飽和電壓為 $\pm 13.5 \text{ V}$

(B) 輸入電壓為直流時 , 此運算放大器的開路電壓增益約為 $100,000$ 倍

(C) 欲使運算放大器進入負飽和

$V_i \geq \frac{13.5}{100000} = 135 \mu\text{V}$

(D) 此電路無負回授 , 虛短路不成立

49. (A) 增益為 0 dB (或增益為 1)時 , 此時的頻率稱為單位增益頻寬 $f = f_{\text{unity}} = 1 \text{ MHz}$

(B) 因 $f_{\text{unity}} = 1 \text{ MHz}$ 為單位增益頻寬 , 所以當頻率為 1 MHz 時 , $V_o = V_i = 10 \text{ mV}_{\text{p-p}}$

(C) 直流增益 $A_0 = 20 \log \left| \frac{-R_2}{R_1} \right| = 20 \text{ dB}$

(D) 此電路最佳工作頻率範圍在 0 至 50 kHz 之間

50. 此電路為反相加法器

$V_{out} = -(V_3 + 0.5V_2 + 0.25V_1 + 0.125V_0)$

輸出電壓的最大值發生在 $V_3 = V_2 = V_1 = V_0 = 1$ 時

$V_{out(\text{max})} = -(1 + 0.5 + 0.25 + 0.125) = -1.875 \text{ V}$