

103 學年度四技二專第五次聯合模擬考試 電機與電子群 專業科目(一) 詳解

103-5-03-4、103-5-04-4

1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16	17	18	19	20	21	22	23	24	25
A	C	D	B	A	D	B	C	B	B	B	A	C	B	D	C	C	D	A	B	B	C	C	C	A
26	27	28	29	30	31	32	33	34	35	36	37	38	39	40	41	42	43	44	45	46	47	48	49	50
A	C	A	B	C	B	B	C	A	B	D	D	A	D	D	B	B	B	D	C	A	C	A	D	C

第一部分：基本電學

1. $V_c = V_{c'}$, $i \cdot X_c = 5i \cdot X_{c'}$, $X_{c'} = \frac{1}{5} X_c$


$\Rightarrow C' = 5C = 5 \times 0.02 \mu = 0.1 \mu F$

$\frac{V}{Z} = i$, $\frac{V}{Z'} = 5i$, $\frac{Z}{Z'} = 5 \Rightarrow Z' = \frac{Z}{5}$

$\sqrt{R'^2 + (\frac{1}{5} X_c)^2} = \frac{\sqrt{(50k)^2 + X_c^2}}{5}$

$(R')^2 + \frac{X_c^2}{25} = \frac{(50k)^2}{25} + \frac{X_c^2}{25}$

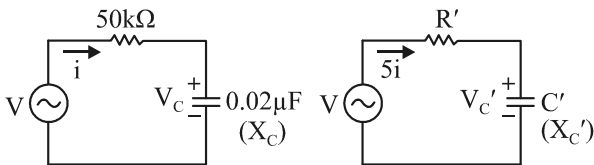$\Rightarrow (R')^2 = \frac{(50k)^2}{25} = 100M \Rightarrow R' = 10k\Omega$



2. $W = \frac{1}{2} LI^2 = \frac{1}{2} \times \frac{NBA}{l} \times I^2$ ($LI = N\phi \Rightarrow L = \frac{N\phi}{I} = \frac{NBA}{l}$)

$= \frac{1}{2} NIBA = \frac{1}{2} FBA = \frac{1}{2} H \cdot l \cdot B \cdot A$

$= \frac{1}{2} \frac{B}{\mu} \times B \times A \times l$ ($A \times l = \text{體積}$)

$= \frac{1}{2} \times \frac{B^2}{\mu} \times A \times l = \frac{1}{2} \times \frac{1.2^2}{4\pi \times 10^{-7}} \times 150 \times 10^{-6} = \frac{270}{\pi}$ 焦耳


3. $I_2 = \frac{Q}{t} = \frac{Q}{\frac{l}{V}} = \frac{Q \times V}{l}$

(V : 速度, l : 距離)

$F = \frac{\mu I_1 I_2 \times l}{2\pi d} = \frac{\mu I_1 \times \frac{QV}{l} \times l}{2\pi d}$

$= \frac{\mu I_1 QV}{2\pi d}$

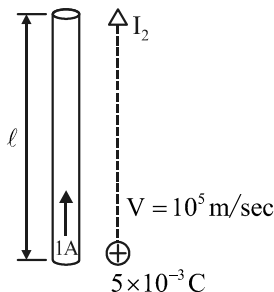$= \frac{4\pi \times 10^{-7} \times 1 \times 5 \times 10^{-3} \times 10^5}{2\pi \times 0.1} = 10^{-3}$ 牛頓



4. 逆電場方向意指電子由低電位移至高電位, 故消耗能量且電位上升

5. 電源切斷表示電容器中的電荷量 Q 已固定則 $Q = Q' \Rightarrow CV = C'V'$, 又電容的距離減半

故 $C' = 2C (C = \epsilon \frac{A}{d})$, 因此 $CV = 2C \times V' \Rightarrow V' = \frac{1}{2} V$

$W = \frac{1}{2} QV = 8$, $W' = \frac{1}{2} Q'V' = \frac{1}{2} \times Q \times \frac{1}{2} V = \frac{1}{4} QV$

$W' = \frac{1}{2} W = \frac{1}{2} \times 8 = 4$ 焦耳

6. $\begin{cases} X_L - X_C = 0 \\ 2X_L - \frac{1}{2} X_C = 45 \end{cases}$

$\frac{3}{2} X_C = 45 \Rightarrow X_C = X_L = 30 \Omega$ (諧振時)

品質因素 $Q_s = \frac{X_L}{R} = \frac{X_C}{R} = \frac{30}{50} = 0.6$

$X_L = \omega L \Rightarrow 100L = 30 \Rightarrow L = 0.3 H$


$X_C = \frac{1}{\omega C} = \frac{1}{100C} = 30 \Rightarrow C = \frac{1}{3} mF$

7. 依據惠斯登電橋實驗結果之推導, $R_x \times \text{負載} = 4 \times 8$, $16 \times \text{負載} = 32$, 故負載電阻值為 2Ω

8. $\alpha_{20} = \frac{1}{222} \Rightarrow \alpha_{20} = \frac{1}{T_0 + 20} \Rightarrow T_0 = 202$

$\frac{T_0 + t_2}{T_0 + t_1} = \frac{R_2}{R_1} \Rightarrow \frac{202 + t_2}{202 + 28} = \frac{150}{10} \Rightarrow t_2 = 3248^\circ C$

9. 將圖中部分電路 $\Delta \rightarrow Y$, 如下圖所示

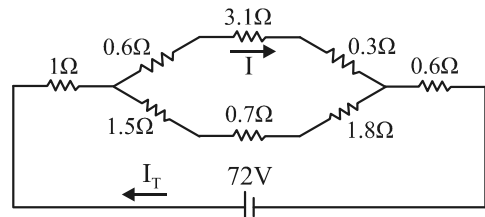

$I_T = \frac{72}{1 + (4 // 4) + 0.6} = 20 A$, $I = 20 \times \frac{4}{4 + 4} = 10 A$


10. 電容穩態 \Rightarrow 開路, 電感穩態 \Rightarrow 短路

$V_c = 4 \Omega$ 上的壓降 $= 60 \times \frac{4}{4 + 8} = 20 V$

11. $V_l = 100\sqrt{3}$, $V_p = \frac{100\sqrt{3}}{\sqrt{3}} = 100 V$ (相電壓)

$I_p = \frac{100}{8 + j6} = 10 A$, $P_\phi = 10^2 \times 8 = 800 W$

$P_{3\phi} = 3 \times 800 = 2400 W$

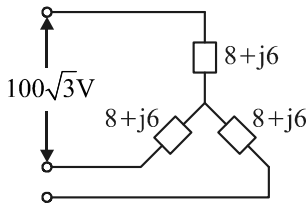

12. 體積不變，拉長 m 倍，面積變為 $\frac{1}{m}$ 倍

$$R = \rho \frac{\ell}{A} \Rightarrow R \propto \frac{\ell}{A}, R' = 10 \times \frac{4}{(\frac{1}{2})^2} = 160 \Omega$$

(線徑 $\frac{1}{n}$ 倍，面積 $\frac{1}{n^2}$ 倍，長度 n^2 倍)


13. 此兩電路分別為電感串聯互助及電感並聯互助
則 $L_s = L_1 + L_2 + 2M = 4 + 8 + 2 \times 1 = 14 \text{ H}$

$$L_p = \frac{L_1 \times L_2 - M^2}{L_1 + L_2 - 2M} = \frac{4 \times 8 - 2^2}{4 + 8 - 2 \times 2} = 3.5 \text{ H}$$


$$\frac{L_s}{L_p} = \frac{14}{3.5} = 4$$

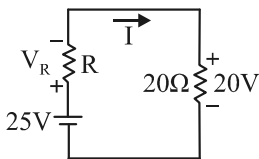14. 開路電壓則為 $E = 25 \text{ V}$ ， $I = \frac{20}{20} = 1 \text{ A}$

$$\text{電阻上的電壓 } V_R = 25 - 20 = 5 \text{ V}, R = \frac{V}{I} = \frac{5}{1} = 5 \Omega$$



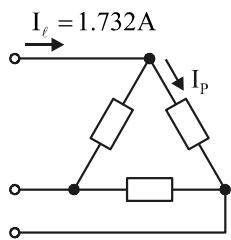15. I_p (相電流) = $\frac{1.732}{\sqrt{3}} \div 1 \text{ A}$



16. $Q = \frac{60 \text{ k}}{0.6} \sqrt{(1^2 - 0.6^2)} = 80 \text{ k}$

$$Q' = \frac{60 \text{ k}}{0.8} \sqrt{1^2 - 0.8^2} = 45 \text{ k}$$

$$Q_c = Q - Q' = 80 \text{ k} - 45 \text{ k} = 35 \text{ kVAR}$$

17. $W_c = \frac{1}{2} QV = \frac{1}{2} CV^2 = \frac{1}{2} \times 50 \mu \times 50^2 = 62.5 \text{ mJ}$

18. $\vec{E}_1 = 9 \times 10^9 \times \frac{2 \times 10^{-8}}{1^2} = 180 \text{ NT/C}$ (向右)


$$\vec{E}_2 = 9 \times 10^9 \times \frac{4 \times 10^{-8}}{2^2} = 90 \text{ NT/C}$$
 (向右)

$$\vec{E} = \vec{E}_1 + \vec{E}_2 = 180 + 90 = 270 \text{ NT/C}$$
 (向右)

$$V_1 = 9 \times 10^9 \times \frac{2 \times 10^{-8}}{1} = 180 \text{ V}$$

$$V_2 = 9 \times 10^9 \times \frac{-4 \times 10^{-8}}{2} = -180 \text{ V}$$
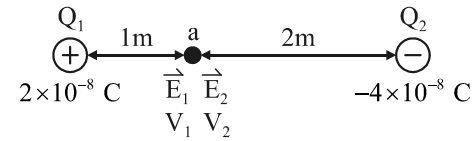
$$V = V_1 + V_2 = 180 + (-180) = 0 \text{ V}$$



19. $F = NI = H\ell$

$$32 \times 6 = H \times 1.6 \Rightarrow H = 120 \text{ AT/m}$$

20. 充電時間常數 $\tau = R \times C = (2 \text{ k} // 2 \text{ k}) \times 5 \text{ m} = 5 \text{ 秒}$

$$V_c \text{ 充電暫態方程式 } V_c(t) = 10(1 - e^{-\frac{t}{\tau}})$$

$$t = 10 \text{ 代入} \Rightarrow V_c(10) = 10(1 - e^{-2}) \doteq 10(1 - 0.135) = 10 \times 0.865 = 8.65 \text{ V}$$

21. $f_0 = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{5 \mu \times 0.5 \text{ m}}} = \frac{1}{2\pi\sqrt{2.5 \times 10^{-9}}} \doteq 3183 \text{ Hz}$


22. 求 R_{AB} 時， R_{CD} 間電阻可拔除視為開路

$$\text{則 } R_{AB} = 2R // 2R // R = 0.5R$$

$$\text{又 } R_{AB} = R_{AC} = R_{CD} = R_{BD} = 0.5R$$

$$\text{因此 } 2R_x = 0.5R \Rightarrow R_x = \frac{1}{4}R = \frac{1}{4} \times 12 = 3 \Omega$$


23. 將電路化為戴維寧等效電路

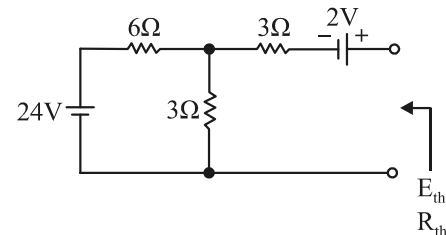

$$R_{th} = (6 // 3) + 3 = 5 \Omega$$

$$E_{th} = 24 \times \frac{3}{6+3} + 2 = 10 \text{ V}$$
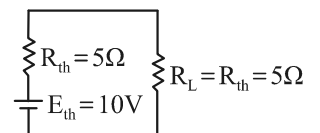
$$P_{max} = \frac{5^2}{5} = 5 \text{ W}$$



24. 利用節點電壓法

$$\frac{V_A - 6}{3} + \frac{V_A}{6} + \frac{V_A - 12}{2} = 0$$


$$\Rightarrow 2V_A - 12 + V_A + 3V_A - 36 = 0$$

$$6V_A = 48 \Rightarrow V_A = 8 \text{ V}$$

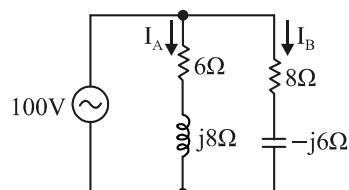25. $I_A = \frac{100}{\sqrt{6^2 + 8^2}} = 10 \text{ A}$ ， $I_B = \frac{100}{\sqrt{8^2 + 6^2}} = 10 \text{ A}$

$$P = 10^2 \times 6 + 10^2 \times 8 = 1400 = 1.4 \text{ kW}$$

$$Q = 10^2 \times 8 - 10^2 \times 6 = 200 = 0.2 \text{ kVar}$$



第二部分：電子學

26. (A) 方波之 $V_{rms} = V_{av}$ ，正弦波之 $V_{rms} = 1.11 V_{av}$ ，三角波之 $V_{rms} = 1.155 V_{av}$ ，故有效值由小到大依序為方波、正弦波、三角波

(B) 平均值與最大値之比

$$V_{av} = \frac{V_m \times T_1 + 0 \times T_2}{T} = \frac{T_1}{T} \times V_m$$

$$\Rightarrow \text{Duty cycle} = \frac{T_1}{T} = \frac{V_{av}}{V_m}$$

(C) 鋸齒波 C.F. = $\sqrt{3} = 1.732$

(D) 半波整流電路 F.F. = $\frac{V_{o(rms)}}{V_{o(av)}} = \frac{\frac{V_m}{2}}{\frac{V_m}{\pi}} = 1.57$

27. $I_{s2} = I_{s1} \times 2^{\frac{T_2 - T_1}{10}} \Rightarrow I_s$ 會隨溫度升高而增加

28. (1) 純矽半導體加入三價鎵原子，每加入一個原子，就會多一帶正電的電洞而形成 P 型半導體


(2) 依摻雜比例可算出電洞濃度

$$P_p = \frac{5 \times 10^{22}}{2 \times 10^8} = 2.5 \times 10^{14} \text{ (電洞/cm}^3\text{)}$$


依質量作用定律 $N_i^2 = p \times n$

$$\text{電子濃度 } n = \frac{N_i^2}{p} = \frac{(1.5 \times 10^{10})^2}{2.5 \times 10^{14}} = 9 \times 10^5 \text{ (電子/cm}^3\text{)}$$


29. (A)

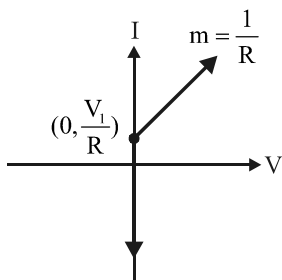

(C)

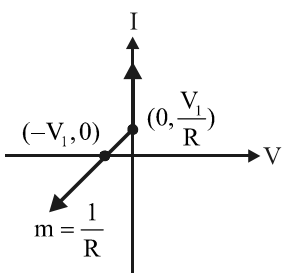

(D)

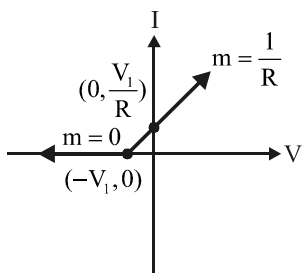

31. $r\% = \frac{2.4}{R_L \times C} \times 100\% = 5.45\%$

32. CB 間順向導通， $V_B = (4 - 0.7) \frac{200 \text{ k}}{200 \text{ k} + 5 \text{ k}} = 3.22 \text{ V}$

$$V_C = 3.22 + 0.7 = 3.92 \text{ V}$$

$$\Rightarrow V_{EB} = -3.22 \text{ (逆偏)}, V_{CB} = 0.7 \text{ V (順偏)}$$

\Rightarrow 電晶體工作在反向主動區

33. 電晶體當成開關使用，當輸入信號 5V 時要確保電晶體進入飽和區，即 $\beta \times I_B \geq I_{C(sat)}$ ，即

$$100 \times \frac{5 - 0.7}{R_B} \geq \frac{10 - 0.2}{0.25 \text{ k}} \Rightarrow R_B \leq 10.97 \text{ k}\Omega$$

34. $I_C = \beta I_B = 50 I_B$ ， $I_E = 51 I_B$ ， $V_E = 51 \text{ k} I_B$

$$V_B = V_{BE} + V_E = 0.7 + 51 \text{ k} I_B$$

$$I_1 = I_2 + I_B = \frac{0.7 + 51 \text{ k} I_B}{10 \text{ k}} + I_B$$

$$I = I_C + I_1 = 51 I_B + \frac{0.7 + 51 \text{ k} I_B}{10 \text{ k}}$$

$$10 = I \times 1 \text{ k} + I_1 \times 100 \text{ k} + V_B$$

$$\Rightarrow 10 = (51 I_B + \frac{0.7 + 51 \text{ k} I_B}{10 \text{ k}}) \times 1 \text{ k}$$

$$+ (\frac{0.7 + 51 \text{ k} I_B}{10 \text{ k}} + I_B) \times 100 \text{ k} + 0.7 + 51 \text{ k} I_B$$

$$\text{解得 } I_B = 3.11 \times 10^{-3} \text{ mA}, I = 0.244 \text{ mA}$$

$$\therefore V_A = 10 - I \times 1 \text{ k} = 9.756 \text{ V}$$

35. 由 Q 點可看出 $I_C = 1.5 \text{ mA}$ ， $V_{CE} = 5 \text{ V}$

$$I_B = \frac{I_C}{\beta} = \frac{1.5 \text{ mA}}{100} = 15 \mu\text{A}$$

$$I_B = \frac{(5 - 0.7)}{R_B}, R_B = 287 \text{ k}\Omega$$

36. $I_C = \alpha I_E = 0.99 \times \frac{5 - 0.7}{1 \text{ k} + \frac{10 \text{ k}}{101}} = 3.87 \text{ mA}$

$$I_{C(sat)} = \frac{15 - 0.2}{1 \text{ k} + 5 \text{ k}} = 2.47 \text{ mA} \leq I_C, \therefore \text{已飽和}$$

$$5 = 10 \text{ k} I_B + 0.7 + (I_B + I_{C(sat)}) \times 1 \text{ k} \dots\dots ①$$

$$15 = 5 \text{ k} I_{C(sat)} + 0.2 + (I_B + I_{C(sat)}) \times 1 \text{ k} \dots\dots ②$$

$$\text{解得 } I_B = 169.23 \mu\text{A}$$

37. $V_B = 10 \times \frac{10 \text{ k}}{40 \text{ k} + 10 \text{ k}} = 2 \text{ V}$ ， $V_E = 2 - 0.7 = 1.3 \text{ V}$


$$I_E = \frac{1.3}{1 \text{ k}} = 1.3 \text{ mA}, r_e = \frac{26 \text{ m}}{1.3 \text{ m}} = 20 \Omega$$

$$A_v = \frac{-(3 \text{ k} // 1 \text{ k})}{20} = -37.5$$

38. $A_i = \left| \frac{I_o}{I_i} \right| = \frac{I_o}{I_e} \times \frac{I_e}{I_b} \times \frac{I_b}{I_i}$

$$= \frac{I_e}{I_e} \times (1 + \beta) \times \frac{I_i \times \frac{270 \text{ k}}{270 \text{ k} + 151 \times 2 \text{ k}}}{I_i} = 71.28$$

39. 高漏電流

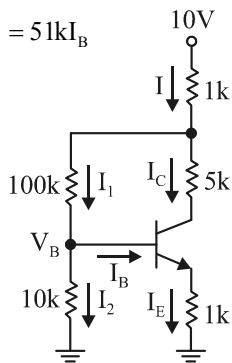

40. $10 \log \frac{32}{2} = 10 \log 2^4 \cong 12 \text{ dB}$
41. $V_{GS} > V_T$ 且 $V_{DS} \geq V_{GS} - V_T$
 $\therefore m = \frac{V_{DS}}{V_{GS} - V_T} \geq 1$ 在第 II 區
42. $0.5I_{DSS} = I_{DSS} \left(1 - \frac{V_{GS}}{V_{GS(off)}}\right)^2 \Rightarrow V_{GS} = 0.293 V_{GS(off)}$
43. 空乏型 MOSFET 工作時，閘極可加正或負偏壓
44. $I_D = 8 \left(1 - \frac{-I_D \cdot 1}{V_{GS(off)}}\right)^2 \Rightarrow I_D = 2 \text{ mA}$
 $g_m = \left| \frac{2}{V_{GS(off)}} \right| \sqrt{I_D \times I_{DSS}} = 2 \text{ mA/V}$
 $A_v = -g_m R_D = -8$
45. $Z_i = 47 \text{ k} // 47 \text{ k} = 23.5 \text{ k}\Omega$
 為一分壓式偏壓共汲極放大電路
 $A_v = \frac{6 \text{ k} // 3 \text{ k}}{\frac{1}{g_m} + 6 \text{ k} // 3 \text{ k}} = 0.5$, $A_i = A_v \times \frac{23.5 \text{ k}}{3 \text{ k}} = 3.92$
46. $R_i = \frac{V_i}{I_i} = \frac{V_i}{\frac{V_i - V_o}{R}} = \frac{V_i}{\frac{V_i - V_i(1 + \frac{R_1}{R_2})}{R}}$
 $= -R \frac{R_2}{R_1} = -100 \text{ k}\Omega$
47. $V_o = -2 \times \frac{10 \text{ k}}{1 \text{ k}} = -20 \text{ V}$ (輸出已經負飽和)
 $\therefore V_o = -15 \text{ V}$
48. $V_o = -RC \frac{dV_i}{dt}$, V_o 電壓與 R 成正比
49. $V_U = \frac{V_{sat} R_1}{R_1 + R_2}$, $V_L = \frac{-V_{sat} R_1}{R_1 + R_2}$
 $\Rightarrow V_H = V_U - V_L = \frac{2V_{sat} R_1}{R_1 + R_2}$
50. $f = \frac{1}{T} = \frac{1}{0.693(R_1 + 2R_2)C}$
 $= \frac{1}{0.693(50 \text{ k} + 2 \times 47 \text{ k})(1 \mu)} \cong 10 \text{ Hz}$