

104 學年度四技二專第三次聯合模擬考試 電機與電子群 專業科目(一) 詳解

104-3-03-4、104-3-04-4

1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16	17	18	19	20	21	22	23	24	25
B	A	C	C	D	C	D	A	A	D	B	D	D	D	C	A	D	B	A	C	A	B	C	B	D
26	27	28	29	30	31	32	33	34	35	36	37	38	39	40	41	42	43	44	45	46	47	48	49	50
B	B	A	D	A	B	B	D	C	D	D	C	A	C	A	A	D	B	A	D	C	C	B	C	C

第一部分：電子學

$$1. V_{av} = \frac{\frac{2}{\pi} \times 10 \times \pi + \frac{2}{\pi} \times (-10) \times \frac{\pi}{2} + \frac{\pi}{2} \times 8 \times \frac{1}{2}}{2\pi} \doteq 2.59 \text{ V}$$

$$2. \text{s.w OFF : } I_{D1} = I_s e^{\frac{V_o}{\eta V_T}}$$

$$\text{s.w ON : } I_{D1} = \frac{I_s}{2} e^{\frac{V_o'}{\eta V_T}}$$

$$\Delta V_o = V_o' - V_o, \quad \frac{I}{2} = e^{\frac{V_o' - V_o}{\eta V_T}}$$

$$\ell_n \frac{1}{2} = \frac{\Delta V_o}{\eta V_T}, \quad \Delta V_o = \eta V_T \times \ell_n \frac{1}{2} \doteq -0.036 \text{ V}$$

$$3. r_z = \frac{\Delta V_z}{\Delta I_z} = \frac{200}{5} = 40 \Omega$$

$$34.5 \times \frac{0.6}{0.3 + 0.6} = 23 (> 5 \text{ V, 二極體崩潰})$$

$$V = \frac{\frac{34.5}{300} + \frac{5}{40}}{\frac{1}{300} + \frac{1}{40} + \frac{1}{600}} = 8 \text{ V}$$

$$I_z = \frac{8 - 5}{40} = 75 \text{ mA} (> I_{ZK}, \text{ 二極體崩潰})$$

$$4. V_{r(p-p)} = 3 \text{ V}, \quad V_{2(p)} = V_{o(dc)} + \frac{V_{r(p-p)}}{2} = 31.5 \text{ V}$$

$$n = \frac{156}{31.5} \doteq 4.95$$

$$5. D_2 \text{ 平均電流 } I_{dc} = \frac{100\sqrt{2} \times \frac{1}{2} \times \frac{1}{\pi}}{1 \text{ k}} \doteq 22.5 \text{ mA}$$

$$6. f_i = 1 \text{ kHz}, \quad T_i = 10^{-3} \text{ sec}, \quad \tau = RC = 10^{-9}$$

$\because T_i \gg \tau, \therefore V_{o(av)} \doteq 0 \text{ V}$

7. BJT 工作於逆向主動區時，CB 接面為順偏 ($V_B > V_E$)，BE 接面為逆偏 ($V_C > V_B$)，故合理選項只有(D)

$$9. I_B = \frac{1}{100 \text{ k}} = 0.01 \text{ mA}, \quad I_E = \frac{10 - 1.7}{5 \text{ k}} = 1.66 \text{ mA}$$

$$(1 + \beta) = \frac{I_E}{I_B} = 166, \quad \beta = 165$$

$$I_C = \beta I_B = 1.65 \text{ mA}$$

$$V_C = -10 + 1.65 \text{ mA} \times 5 \text{ k} = -1.75 \text{ V}$$

$$12. I_E = \frac{10 - 0.7}{\frac{900 \text{ k}}{100} + 0.3 \text{ k}} = 1 \text{ mA} \doteq I_C$$

$$g_m = \frac{I_C}{V_T} = 40 \text{ mA/V}$$

$$13. I_B \doteq \frac{10.7 - 0.7}{100 \text{ k} + 7.5 \text{ k} \times 120} = 0.01 \text{ mA}$$

$$I_C = \beta I_B = 1.2 \text{ mA}$$

$$A_i = 120 \times \frac{7.5 \text{ k}}{7.5 \text{ k} + 15 \text{ k}} = 40$$

$$r_\pi = \frac{V_T}{I_B} = \frac{25 \text{ m}}{0.01 \text{ m}} = 2.5 \text{ k}\Omega$$

$$A_v = \frac{120 \times (7.5 \text{ k} // 15 \text{ k})}{100 \text{ k} + 2.5 \text{ k} + 120 \times (7.5 \text{ k} // 15 \text{ k})} \doteq 0.85$$

$$14. A_{p(dB)} = 20 \log |A_v| + 10 \log \frac{R_i}{R_L}$$

$$= 20 \log |-100| + 10 \log \frac{100 \text{ k}}{10} = 80 \text{ dB}$$

$$15. -3 \text{ dB 處之電壓增益為 } \frac{150}{\sqrt{2}} \doteq 106$$

$$16. A_i = \beta_1 \times \beta_2 = 900$$

$$R_i \doteq \beta_1 \times \beta_2 \times 1 \text{ k} = 900 \text{ k}\Omega$$

$$17. R_D = \frac{3}{0.5 \text{ m}} = 6 \text{ k}\Omega, \quad I_D = k(V_{GS} - V_t)^2$$

$$0.5 \text{ m} = 0.5 \text{ m}(V_{GS} + 1)^2, \quad V_{GS} = -2 \text{ V}$$

$$V_{GS} = 0 \text{ V (不合理)}$$

$$R_{G1}、R_{G2} \text{ 之合理值為 } 2 \text{ M}\Omega、3 \text{ M}\Omega$$

$$19. R = \frac{0.7}{0.1 \text{ m}} = 7 \text{ k}\Omega$$

20. 共閘極放大之輸入阻抗很小，輸出阻抗很大，電壓增益很大，輸入與輸出訊號同相

$$21. A_v = -g_m(R_D // R_L) = -0.5 \times (10 \text{ k} // 10 \text{ k}) = -2.5$$

23. μA741 開迴路增益約為 10^5

$$24. \text{S.R.} \triangleq \frac{\Delta V_o}{\Delta t}, \text{ 當訊號為弦波時}$$


$$f_{o(max)} \leq \frac{\text{S.R.}}{2\pi V_m}, \quad f_{o(max)} \leq \frac{0.5 \text{ V}/\mu\text{s}}{2\pi \times 5}, \quad f_{o(max)} \leq 15.9 \text{ kHz}$$

$$25. R_1 = R_2 = R, \quad R_3 = R_4 = R', \quad R_5 = R_6 = R_f$$


$$V_o = \frac{R_f}{R'}(1 + \frac{2R}{R_G})(V_+ - V_-) = \frac{100 \text{ k}}{50 \text{ k}}(1 + \frac{2 \times 40 \text{ k}}{20 \text{ k}})(5 - 3) = 20 \text{ V}$$

第二部分：基本電學

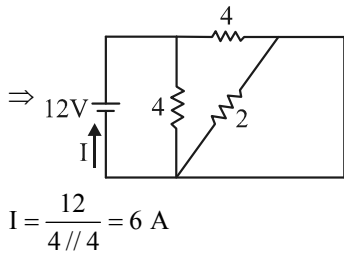26. (B) 電壓調整率越小越好，理想為零
 27. (B) 導線間相互吸引
 28. $M = K\sqrt{L_1 L_2} = 0.5 \times \sqrt{9 \times 4} = 3$
 $L_t = L_1 + L_2 + 2M = 19 \text{ mH}$
 29. (A) i_1 落後 i_2 30°
 (B) $i_1 = \frac{20}{\sqrt{2}} \angle 30^\circ = 10\sqrt{2} \angle 30^\circ$
 $= 10\sqrt{2} \cos 30^\circ + j10\sqrt{2} \sin 30^\circ = 5\sqrt{6} + j5\sqrt{2}$
 (C) $i_{\text{rav}} = 20 \times \frac{2}{\pi} = \frac{40}{\pi} \approx 12.7 \text{ V}$
 (D) $W = 314 = 2\pi f$, $f = 50 \text{ Hz}$, $T = 0.02 \text{ s}$
 時間差 $30^\circ \Rightarrow 0.02 \times \frac{30}{360} = \frac{1}{600} \text{ s}$
 30. $W = CV^2$, $8 = C \times 200^2$, $C = 200 \mu\text{F}$
 (電源提供之電能， $W = QV = CV^2$ ，電容儲存能量為電源提供之一半)
 31. 瞬間電容短路，電感開路




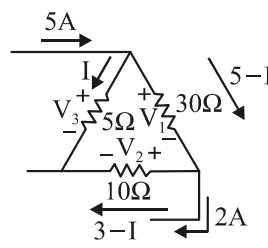32. $100 \text{ V} / 200 \text{ W} \Rightarrow R = \frac{V^2}{P} = \frac{100^2}{200} = 50 \Omega$
 均勻拉長， $l' = 2l$ ，體積不變
 $\therefore A' = \frac{1}{2} A$, $R' = \rho \cdot \frac{2l}{\frac{1}{2} A} = 4R$
 剪成 2 段並聯， $2R // 2R = R = 50 \Omega$
 $P = \frac{100^2}{50} = 200 \text{ W}$
 33. $V_1 + V_2 = V_3$
 $30(5 - I) + 10(3 - I) = 5I$
 $180 = 45I$
 $I = 4 \text{ A}$
 34. $W = 1000$, $X_C = \frac{1}{WC} = 40$
 $Z = R - jX_C = 30 - j40 = 50 \angle -53^\circ$
 $\bar{I} = 2 \angle 23^\circ$, $\bar{E} = \bar{I}Z = 100 \angle -30^\circ$
 35. $R_{\text{th}} = 5 + 5 = 10$, 開路電壓 $E_{\text{th}} = 25 + 5 \times 5 = 50$
 R_L 最大功率




$$P = \frac{E_{\text{th}}^2}{4R_{\text{th}}} = \frac{2500}{40} = 62.5 \text{ W}$$

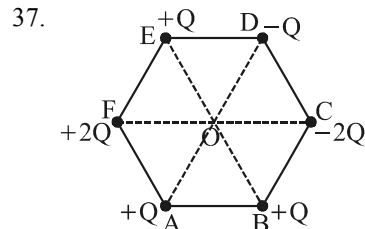36. 棕、紅、綠、棕、紅 $\Rightarrow 125 \times 10^1 \pm 2\% \Omega$
 $I = \frac{10}{1.25 \text{ k}} = 8 \text{ mA} = nevA$
 $8 \times 10^{-3} = 10^{29} \times 1.6 \times 10^{-19} \times v \times 5 \times 10^{-6}$
 $v = 10^{-7} \text{ m/s}$






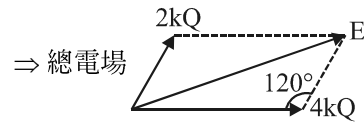B、E 二點之電場抵消
 A、D 二點產生之電場大小均為 $\frac{kQ}{l^2}$ ，方向為 ↗
 C、F 二點產生之電場大小均為 $\frac{2kQ}{l^2}$ ，方向為 →



$$E = \sqrt{2^2 + 4^2 - 2 \cdot 2 \cdot 4 \cos 120^\circ} kQ = 2\sqrt{7} kQ$$

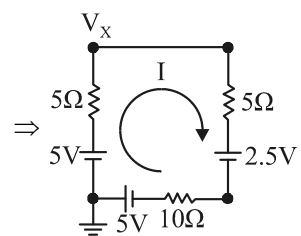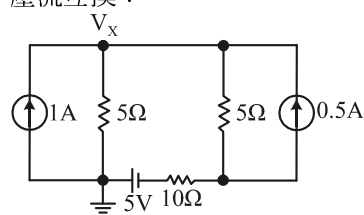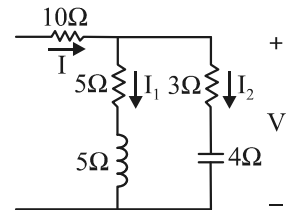38. $Z_1 = 5 + 5j = 5\sqrt{2} \angle 45^\circ$
 $Z_2 = 3 - 4j = 5 \angle -53^\circ$
 $V = \bar{I}_1 Z_1 = \bar{I}_2 Z_2 = 100 \angle 0^\circ$
 $\Rightarrow \bar{I}_1 = 10\sqrt{2} \angle -45^\circ$
 $\bar{I} = \bar{I}_1 + \bar{I}_2$
 $= 10 - j10 + 12 + j16$
 $= 22 + j6$
 39. 壓流互換：




$$I = \frac{7.5}{20} = 0.375 \text{ A} , V_x = 5 - 0.375 \times 5 = 3.125 \text{ V}$$

$$\therefore I_1 = \frac{3.125}{10} = 0.3125 \text{ A}$$

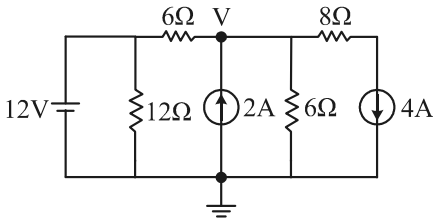40. 密爾門： $V = (\frac{12}{6} + 2 - 4) \times (6 // 6) = 0 \text{ V}$

$\therefore P_{2A} = 2 \times 0 = 0 \text{ W}$



41. $V_{av} = \frac{\frac{2 \times 2}{2} + 4 \times 1 + (-4 \times 1) + \frac{2 \times 1}{2}}{5} = 0.6 \text{ V}$

$V_{rms} = \sqrt{\frac{(\frac{2}{\sqrt{3}})^2 \times 2 + 4^2 \times 2 + (\frac{2}{\sqrt{3}})^2 \times 1}{5}} = \frac{6}{5} \sqrt{5} \text{ V}$

42. $V(t) = 100 \sin(314t + 60^\circ)$

$P_{max} = EI(\cos \theta + 1) = \frac{100}{\sqrt{2}} \times \frac{20}{\sqrt{2}} (\cos 30^\circ + 1)$
 $= 1000 \times 1.866 = 1866 \text{ W}$

43. $Q = \frac{100}{\sqrt{2}} \times \frac{20}{\sqrt{2}} \times \sin 30^\circ = 500 \text{ Var}$

$500 = \frac{E^2}{X_C}, X_C = \frac{E^2}{500} = \frac{(\frac{100}{\sqrt{2}})^2}{500} = 10 = \frac{1}{WC} = \frac{1}{314C}$

$\Rightarrow C = \frac{1}{3140} \doteq 318 \mu\text{F}$

44. $W = QV = Pt, 1810 \times 3.8 = P \times 14, P \doteq 491 \text{ mW}$

45. $W = \frac{1}{2} \frac{Q^2}{C}, 45 \text{ m} = \frac{1}{2} \times \frac{Q^2}{4 \times 10^{-6}}, Q = 6 \times 10^{-4} \text{ C}$

並上 AB 後，電壓降為 75 V

$Q = (C_{AB} + 4 \mu) \times V, 6 \times 10^{-4} = (C_{AB} + 4 \mu) \times 75$


$C_{AB} = 4 \mu$

$C_{CD} = \frac{6 \times 4}{6 + 4} + 0.6 = 3 \mu$


$C_{BE} = \frac{3 \times 6}{3 + 6} + 3 = 5 \mu$

$C_{AB} = \frac{5 \times C_6}{5 + C_6} = 4$

$20 + 4C_6 = 5C_6, C_6 = 20 \mu\text{F}$

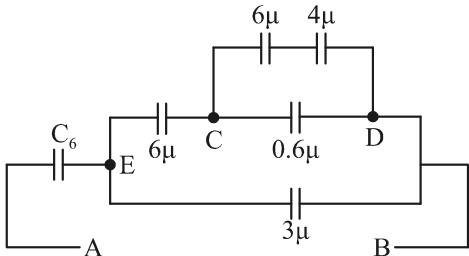

46.

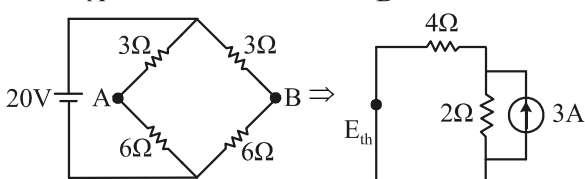

\Rightarrow AB 看入之戴維寧

\Rightarrow 滿足惠斯登電橋 $E_{th} = 0$


$R_{th} = (3 // 6) + (3 // 6) = 4 \Omega$

$\therefore I_{2\Omega} = 3 \times \frac{4}{2 + 4} = 2 \text{ A}$


47. $R_{20} = \rho \cdot \frac{\ell}{A} = 3.5 \times 10^{-5} \times \frac{0.5}{10^{-4}} = 0.175 \Omega$

$\Rightarrow \alpha_0 = \frac{1}{180}, \frac{R_{80}}{R_{20}} = \frac{|T_0| + 80}{|T_0| + 20} = \frac{260}{200} = \frac{R_{80}}{0.175}$
 $T_0 = -180$

$R_{80} = 0.2275 \Omega$

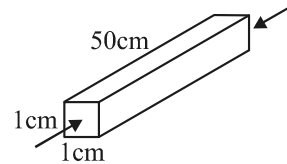

48. 由中垂線對稱法

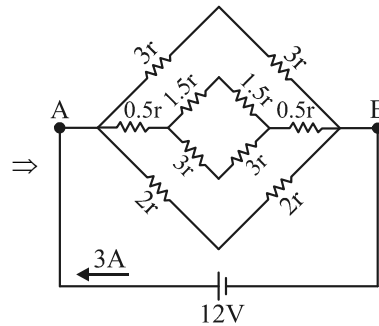

$\therefore R_{AB} = 6r // (0.5r + 3r // 6r + 0.5r) // 4r$

$= 6r // 3r // 4r = \frac{12}{9} r = \frac{4}{3} r$

$\Rightarrow R_{AB} = \frac{12}{3} = 4 = \frac{4}{3} r \Rightarrow r = 3 \Omega$

49. S 撥至 1 $V(t) = 12 + (0 - 12)e^{-\frac{t}{2m}}$
 $V(4ms) = 12 - 12e^{-2}$

S 撥至 2 $V'(t) = -12 + (12 - 12e^{-2} + 12)e^{-\frac{t}{4m}}$
 $V(4ms) = -12 + 24e^{-1} - 12e^{-3}$

50. $Z = 10\sqrt{5} \angle \tan^{-1} 2 = 10 + j20$

$Y = \frac{1}{Z} = \frac{1}{10 + j20} = \frac{10 - j20}{500} = \frac{1}{50} - j\frac{1}{25}$

$\Rightarrow R = 50, X_L = 25$

$\omega \rightarrow 2\omega, \therefore X_L' = 50$

串聯 $Z' = 50 + j50 = 50\sqrt{2} \angle 45^\circ$

$\bar{E} = 100 \angle 0^\circ, \bar{I} = \frac{\bar{E}}{Z} = \sqrt{2} \cdot \angle -45^\circ$