

104 學年度四技二專第五次聯合模擬考試 電機與電子群 專業科目(一) 詳解

104-5-03-4、104-5-04-4


1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16	17	18	19	20	21	22	23	24	25
C	B	D	A	B	C	A	C	A	D	B	C	A	D	B	C	A	C	B	A	D	C	A	B	B
26	27	28	29	30	31	32	33	34	35	36	37	38	39	40	41	42	43	44	45	46	47	48	49	50
B	A	D	C	C	A	B	D	B	D	A	C	A	B	D	C	B	A	C	A	B	C	D	C	D

第一部分：電子學

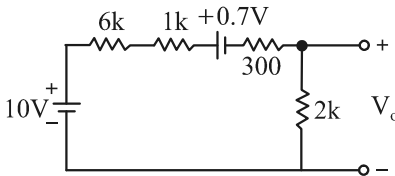1. (C) 價電子位於原子核之最外層軌道上，當變成爲自由電子時，爲吸收能量

$$2. \frac{i_{o2}}{i_{o1}} = 2^N = 2^{\frac{1}{2}} = \sqrt{2} \quad (\because N = \frac{\Delta T}{10} = \frac{5}{10} = \frac{1}{2})$$

$$3. V_o = (10 - 0.7) \times \frac{2}{6 + 1 + 2 + 0.3} = 9.3 \times \frac{2}{9.3} = 2 \text{ V}$$



$$4. V_{2m} = \frac{50\sqrt{2}}{10} = 5\sqrt{2} \text{ V}$$

$$\therefore V_{RL} = \frac{5\sqrt{2}}{\pi} \times \frac{2}{0.5 + 2} = 1.8 \text{ V}$$

$$\therefore P_L = \frac{V_{RL}^2}{R_L} = \frac{1.8^2}{2 \text{ k}} = 1.62 \text{ mW}$$

$$5. PIV = 2V_{2m}' = 10\sqrt{2} \text{ V}$$

$$\therefore V_{2m}' = 5\sqrt{2} \text{ V} \Rightarrow V_{2m} = 2V_{2m}' = 10\sqrt{2}$$

$$\therefore \frac{V_{im}}{V_{2m}} = \frac{5}{1} \Rightarrow V_{im} = 5 \times 10\sqrt{2} = 50\sqrt{2}$$

$$\therefore V_i(t) = 50\sqrt{2} \sin \omega t$$

6. $V_i = -5 \text{ V} \Rightarrow D_2 \text{ on, } D_1 \text{ off}$

$$V_o = (-5 + 2) \times \frac{5}{10 + 5} + (-2)$$

$$= (-3) \times \frac{1}{3} - 2 = -1 - 2 = -3 \text{ V}$$

7. (A) 降低基極寬度與提高射極雜質濃度，可提高電晶體放大倍率

$$8. \beta = \frac{\alpha}{1 - \alpha} = \frac{0.98}{1 - 0.98} = 49$$

$$\beta' = \frac{0.96}{1 - 0.96} = 24$$

$$\Delta\beta = 49 - 24 = 25$$

9. $V_{CE} \approx 0.2 \text{ V}$

10. ① $R_B = 40 \text{ k} // 10 \text{ k} = 8 \text{ k}\Omega$

$$V_B = 10 \times \frac{10}{40 + 10} = 2 \text{ V}$$

$$\textcircled{2} I_B = \frac{10 - 0.7 - 2}{8}$$

$$\approx 0.91 \text{ mA}$$

$$I_{C(\text{sat})} = \frac{10 - 0.2}{0.8} = 12.25 \text{ mA}$$

$$I_{B(\text{min})} = \frac{I_{C(\text{sat})}}{50} = 0.245 \text{ mA}$$

$\therefore I_B > I_{B(\text{min})}$ ， \therefore BJT 飽和， $\therefore I_C = I_{C(\text{sat})} = 12.25 \text{ mA}$

11. ① $(12 - 0.7) = (1 + 100)I_B \times 2 + 150I_B + (1 + 100)I_B \times 1$

$$\Rightarrow I_B = \frac{11.3}{453} \approx 0.025 \text{ mA}$$

$$\therefore r_\pi = \frac{V_T}{I_B} = \frac{25}{0.025} = 1 \text{ k}\Omega$$

$$\textcircled{2} \frac{V_o}{V_i} = \frac{V_o}{V_b} \times \frac{V_b}{V_i} = -100 \times \frac{(75 // 2)}{1} \times \frac{(75 // 1)}{(75 // 1) + 1.5}$$

$$\approx -100 \times 2 \times 0.4 = -80$$

$$12. A_i = \frac{I_o}{I_i} = \frac{I_o}{i_c} \times \frac{i_c}{i_b} \times \frac{i_b}{I_i}$$

$$= 1 \times 150 \times \frac{(36 // 4)}{(36 // 4) + 2} \approx 150 \times 0.64 = 96$$

$$13. \alpha = \frac{49}{1 + 49} = 0.98, \quad r_e = \frac{1.5 \text{ k}}{1 + 49} = 30 \Omega$$

$$\therefore A_v = \alpha \times \frac{Z_L}{r_e} = 0.98 \times \frac{(10 \text{ k} // 90 \text{ k})}{30} = 294$$

$$16. 20 \text{ dBm} = 10 \log \frac{P_o}{1 \text{ m}} \Rightarrow P_o = 100 \text{ mW}$$

$$\Rightarrow 100 \text{ m} = I_o^2 \times 10 \Rightarrow I_o = 0.1 \text{ A}$$

$$18. \textcircled{1} V_{GS} = 16 \times \frac{1.5}{4.5 + 1.5} - 2I_D = (4 - 2I_D)$$

$$\textcircled{2} I_D = 4 \times \left(1 - \frac{4 - 2I_D}{-2}\right)^2 = 4 \times (3 - I_D)^2$$


$$\Rightarrow 4I_D^2 - 25I_D + 36 = 0$$

$$\Rightarrow I_D = 2.25 \text{ mA} \text{ 或 } 4 \text{ mA (不合)}$$

$$\therefore V_D = 16 - 2.25 \times 4 = 7 \text{ V}$$

$$19. \textcircled{1} V_{GS} = V_{DS} = 5 - 5I_D$$
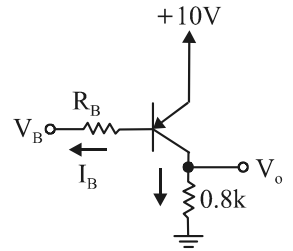
$$\textcircled{2} I_D = 0.6 \times (5 - 5I_D - 1)^2$$



$$\Rightarrow I_D = 0.6 \text{ mA 或 } 1.06 \text{ mA (不合)}$$

$$\textcircled{3} g_m = 2 \times 0.6 \times [(5 - 5 \times 0.6) - 1] = 1.2 \text{ mA/V}^2$$

$$\textcircled{4} A_v = \frac{V_o}{V_s} = -g_m \times (R_D // R_L) = -1.2 \times (5 // 5) = -3$$

$$20. \text{ 當 } R_1 = 10 \text{ k} , R_2 = 15 \text{ k}$$

$$V_o = 7.5 \text{ V} = \left(\frac{R_2}{R_1}\right) \times (10 - 5) , \therefore \frac{R_2}{R_1} = 1.5$$

$$21. \textcircled{1} t = 0 \sim 2 \text{ ms}$$

$$V_o = -(0.1 \mu \times 5 \text{ k}) \times \frac{20}{2 \text{ ms}} = -5 \text{ V}$$

$$\textcircled{2} t = 2 \sim 4 \text{ ms}$$

$$V_o = -(0.1 \mu \times 5 \text{ k}) \times \frac{0 - 20}{(4 - 2) \text{ ms}} = +5 \text{ V}$$

$$\textcircled{3} V_{o(p-p)} = 5 - (-5) = 10 \text{ V}$$

$$22. \textcircled{1} V_H = 2 \times V_{\text{sat}} \times \frac{R_2}{R_1}$$

$$\Rightarrow 12 = 2 \times V_{\text{sat}} \times \frac{5}{10} \Rightarrow V_{\text{sat}} = 12 \text{ V}$$

$$\textcircled{2} V_{UT} = 10.5 = V_R \times \frac{10 + 5}{10} + \frac{5}{10} \times 12 \Rightarrow V_R = 3 \text{ V}$$

$$24. f = \frac{1}{2 \cdot R \cdot C \times \ln\left(1 + \frac{2R_2}{R_1}\right)}$$

$$= \frac{1}{2 \times 10 \text{ k} \times 1 \mu\text{F} \times \ln\left(1 + \frac{2 \times 10}{5}\right)} = 31.25 \text{ Hz}$$

$$25. V_{UT} = +15 \text{ V} \times \frac{R_2}{R_1 + R_2} = 15 \times \frac{10}{10 + 5} = 10 \text{ V}$$

第二部分：基本電學

$$26. I = \frac{Q}{t} = \frac{5 \times 10^5 \times 1.6 \times 10^{-19}}{1 \times 10^{-9}} = 8 \times 10^{-5} \text{ A}$$

$$P = I^2 \times R = (8 \times 10^{-5})^2 \times 100 \text{ k} = 0.64 \text{ mW}$$

$$27. W = Pt = Q \times V$$

$$\Rightarrow t = \frac{Q \times V}{P} = \frac{50 \times 3600 \times 2 \times 12}{20}$$

$$= 216000 \text{ s} = 60 \text{ hrs}$$

$$28. R' = \rho \cdot \frac{\frac{1}{2} \ell}{\left(\frac{2}{1.6}\right)^2 \text{ A}} = \frac{1}{2} \times \frac{16}{25} \rho \cdot \frac{\ell}{\text{A}} = \frac{8}{25} R$$

$$\therefore R' = \frac{8}{25} \times 2.5 = 0.8 \Omega$$

$$29. R = 20 \times 10^3 \Omega \pm 10\% \Rightarrow R_{\text{max}} = 22 \text{ k}\Omega$$

$$\therefore P_{\text{max}} = (10 \times 10^{-3})^2 \times R_{\text{max}} = 2.2 \text{ W}$$

$$30. \text{ 令 } R_1 = 2R , R_2 = 3R , R_3 = 6R$$

$$\therefore I_{R_3} = \frac{2 \times R_2}{R_3} = \frac{2 \times 3R}{6R} = 1 \text{ A}$$


$$\Rightarrow I_T = I_{R_1} = 2 + 1 = 3 \text{ A}$$

$$\therefore R_T = \frac{120 \text{ V}}{I_T} \Rightarrow R_1 + (R_2 // R_3) = \frac{120}{3}$$

$$\Rightarrow 4R = 40 \Rightarrow R = 10$$

$$\therefore P_{R_3} = I_{R_3}^2 \times R_3 = 1^2 \times (6 \times 10) = 60 \text{ W}$$

31. 原圖

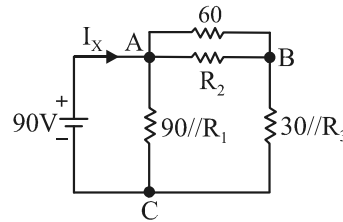

$$R_1 = \frac{60 \times 30 + 60 \times 20 + 20 \times 30}{20} = \frac{3600}{20} = 180 \Omega$$

$$R_2 = \frac{3600}{30} = 120 \Omega , R_3 = \frac{3600}{60} = 60 \Omega$$

$$I_x = \frac{90}{90 // R_1 // [(60 // R_2) + (30 // R_3)]} = \frac{90}{30} = 3 \text{ A}$$

$$32. P_{5\Omega} = \left(\frac{12 - 6}{5}\right)^2 \times 5 = 7.2 \text{ W}$$

$$33. \textcircled{1} R_L = 1 + (6 // 12) = 5 \Omega$$

$$\textcircled{2} 2 \text{ A 開路} : I' = \frac{36}{12 + (6 // 6)} \times \frac{6}{6 + 6} = \frac{6}{5} \text{ A}$$

$$\textcircled{3} 36 \text{ V 短路} : I'' = (-2) \times \frac{(6 // 12)}{6 + (6 // 12)} = -\frac{4}{5} \text{ A}$$

$$\therefore I = I' + I'' = \frac{2}{5} \text{ A} = 0.4 \text{ A}$$

$$34. \textcircled{1} C_T = \frac{600 \times (100 + 200)}{600 + (100 + 200)} = 200 \mu\text{F}$$

$$\textcircled{2} Q_T = 100 \mu \times 100 + 200 \mu \times 50 = 20000 \mu\text{C}$$

$$V = \frac{Q_T}{C_T} = 100 \text{ V}$$

$$35. W = \frac{1}{2} \times C_T \times 50^2 = \frac{1}{2} \times 200 \mu\text{F} \times 2500 = 2500 \times 10^{-4} = 0.25 \text{ J}$$

$$36. \text{(B)} L' = \frac{\mu\text{A} \cdot \left(\frac{1}{2} \text{ N}\right)^2}{\frac{1}{2} \ell} = \frac{1}{2} \frac{\mu\text{A} \cdot \text{N}^2}{\ell} = \frac{1}{2} \times L = 5 \text{ H}$$

$$\text{(C)} L' = \frac{\mu \times (2\text{A}) \cdot (2\text{N})^2}{\ell} = 8 \frac{\mu\text{A} \cdot \text{N}^2}{\ell} = 8 \times L = 80 \text{ H}$$


$$\text{(D)} L' = \frac{\mu \left(\frac{1}{2} \text{ A}\right) \cdot \left(\frac{1}{2} \text{ N}\right)^2}{\ell} = \frac{1}{8} \frac{\mu\text{A} \cdot \text{N}^2}{\ell} = \frac{1}{8} \times L = 1.25 \text{ H}$$

$$37. \textcircled{1} L_A = N_A \cdot \frac{\phi_A}{I_A} \Rightarrow 8 = N_A \times \frac{8 \times 10^{-1}}{10} \Rightarrow N_A = 100 \text{ 匝}$$

$$\textcircled{2} K = \frac{5 \times 10^{-1}}{8 \times 10^{-1}} = \frac{5}{8} , M = N_B \times \frac{5 \times 10^{-1}}{10}$$

$$\textcircled{3} N_B \times \frac{5 \times 10^{-1}}{10} = \frac{5}{8} \times \sqrt{8 \times 72} = 15 , \therefore N_B = 300 \text{ 匝}$$

38. 原圖

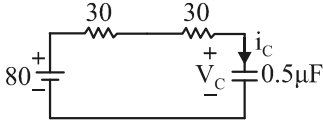


① $\tau = (30 + 30) \times 0.5 \mu = 30 \mu\text{s}$

② $V_c(t) = 80 \times (1 - e^{-\frac{t}{30\mu}})$

$\Rightarrow V_c(60 \mu\text{s}) = 80 \times (1 - 0.135) = 69.2 \text{ V}$

③ $i_c(60 \mu\text{s}) = \frac{80 - V_c(60 \mu\text{s})}{60} = 0.18 \text{ A}$

39. 原圖(S→①)

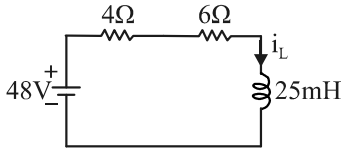

(1) $t = 0 \text{ s}$, $S \rightarrow \textcircled{2}$, $i_L(0^+) = \frac{48}{4 + 6} = 4.8 \text{ A}$

(2) $I = 4.8 \times \frac{12}{12 + 6} = 3.2 \text{ A}$

40. $F.F_{\text{三角波}} = \frac{2}{\sqrt{3}} \doteq 1.16$

$F.F_{\text{正弦波}} = \frac{\pi}{2\sqrt{2}} \doteq 1.11$

$F.F_{\text{方波}} = 1$

41. ① $\bar{V}_1 = \frac{20}{\sqrt{2}} \angle 60^\circ$, $\bar{V}_2 = \frac{20}{\sqrt{2}} \angle 120^\circ$

② $\bar{V}_A = \bar{V}_1 + \bar{V}_2 = j \frac{20}{\sqrt{2}} \times \sqrt{3}$

$\Rightarrow V_A(t) = 20\sqrt{3} \sin(314t + 90^\circ) = 20\sqrt{3} \cos 314t$

③ $\bar{V}_B = \bar{V}_1 - \bar{V}_2 = \frac{20}{\sqrt{2}} \Rightarrow V_B(t) = 20 \cdot \sin 314t$

42. $i_c(t) = \sqrt{2} \cdot \sin(500t + 67^\circ) \Rightarrow \bar{I}_C = 1 \angle 67^\circ = \bar{I}$

$\bar{Z} = \frac{\bar{V}_s}{\bar{I}} = \frac{100 \angle 30^\circ}{1 \angle 67^\circ} = 100 \angle -37^\circ$

$= 80 - j60 = 80 + j100 - jX_C$

$\Rightarrow X_C = 160 \Omega = \frac{1}{500 \times C} \Rightarrow C = 12.5 \mu\text{F}$

43. ① $\bar{I}_1 = 5 \angle -53^\circ \times \frac{j30}{40 + j30} = 3 \angle 0^\circ = 3$

② $\bar{I}_2 = \frac{10}{\sqrt{2}} \angle 37^\circ \times \frac{-j4}{4 - j4} = 5 \angle -8^\circ$

③ $\frac{|I_1|}{|I_2|} = \frac{3}{5} = 0.6$

44. $\bar{V} = \frac{100}{\sqrt{2}} \angle -30^\circ$, $\bar{I} = \frac{50}{\sqrt{2}} \angle 30^\circ$ 超前

$P_{\text{max}} = VI \cdot (\cos 60^\circ + 1) = 3750 \text{ W}$

45. ① $\bar{Z} = j50 + (50 + j50) // (50 - j50)$
 $= 50 + j50 = 50\sqrt{2} \angle 45^\circ \Omega$

② $I_{\text{dc}} = \frac{200}{50} = 4 \text{ A}$ (C→開路, L 短路)

③ $\bar{I}_{\text{AC}} = \frac{200}{50\sqrt{2}} \angle 0^\circ = 2 \angle -45^\circ \text{ A}$

$\Rightarrow i_{\text{ac}}(t) = 2\sqrt{2} \sin(100t - 45^\circ) \text{ A}$

④ $i_{(t)} = 4 + i_{\text{ac}}(t) = 4 + 2\sqrt{2} \sin(100t - 45^\circ) \text{ A}$

46. $\bar{I}_1 = \frac{120 \angle 0^\circ}{6 + j8} = 12 \angle -53^\circ \text{ A}$

$\bar{I}_2 = \frac{120 \angle 0^\circ}{8 - j6} = 12 \angle +37^\circ \text{ A}$

$Q_L = I_1^2 \times 8$, $Q_C = I_2^2 \times 6$

$\therefore Q_T = Q_L - Q_C = 12^2 \times (8 - 6) = 288 \text{ VAR}$

47. $X_{L0} = 2\pi f_0 L = 10$, $Q = \frac{X_{L0}}{R} = \frac{10}{2.5} = 4$

$\therefore BW = \frac{f_0}{Q} = \frac{10^3}{4} = \frac{125}{\pi} \text{ Hz}$

48. (A) RLC 串並聯諧振電路中, Q 為電抗功率與平均功率之比值

(B) $Q = \frac{1}{R} \times \sqrt{\frac{L}{C}}$

(C) 成反比

49. $V_p = \frac{V_\ell}{\sqrt{3}} = \frac{150}{\sqrt{3}} \text{ V}$

$I_p = \frac{V_p}{30 + j40} = \frac{150}{50 \angle 53^\circ} = \sqrt{3} \angle -53^\circ \text{ A}$

$Q_T = 3V_p \cdot I_p \cdot \sin 53^\circ = 3 \times \frac{150}{\sqrt{3}} \times \sqrt{3} \times \frac{4}{5} = 360 \text{ VAR}$

50. $\text{PF} = \cos 53^\circ = 0.6$ 滯後