

# 101 學年四技二專第二次聯合模擬考試 電機與電子群 專業科目 (一) 詳解

101-2-03-4  
101-2-04-4

1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16	17	18	19	20	21	22	23	24	25
C	B	D	B	A	B	D	B	A	D	D	A	C	C	A	D	B	A	D	C	A	C	C	D	B
26	27	28	29	30	31	32	33	34	35	36	37	38	39	40	41	42	43	44	45	46	47	48	49	50
B	C	D	B	C	B	A	C	D	A	B	A	D	C	C	D	A	B	C	A	D	C	B	A	C

### 第一部份：基本電學

1.  $\$ = 220 \times 2 + 440 \times 2.5 + 100 \times 3.2 = 1,860$  元

2.  $I_1$  迴路： $R_1 + R_2 + R_3 = 7 \Omega$ ， $R_2 = 2 \Omega$

$R_3 = 1 \Omega \Rightarrow R_1 = 4 \Omega$


$I_3$  迴路： $R_4 = 3 \Omega$ ， $R_3 + R_4 + R_5 = 6 \Omega \Rightarrow R_5 = 2 \Omega$

$\therefore R_1 + R_3 + R_5 = 4 + 1 + 2 = 7 \Omega$

3.  $I_T = \frac{5V}{R_T} = \frac{5}{\frac{10}{50}} = 25A$

4.  $I = \frac{120}{2.4 + (4+12) \parallel (6+18)} \times \frac{16}{16+24} = 4A$

$P_{6\Omega} = 4^2 \times 6 = 96W$

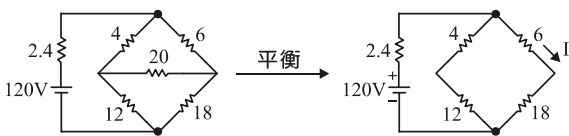

5.  $90Ah = I \times \frac{720}{60} \Rightarrow I = 7.5A$

6. 馬力(hP)：功率單位

7.  $R = \rho \cdot \frac{l}{A}$ ， $l_1 \cdot A_1 = l_2 \cdot (\frac{1}{2})^2 \cdot A_1 \Rightarrow l_2 = 4l_1$

$\frac{R_1}{R_2} = \frac{\frac{l_1}{A_1}}{\frac{4l_1}{(\frac{1}{2})^2 \cdot A_1}} = \frac{1}{16} \Rightarrow \frac{G_2}{G_1} = \frac{1}{16}$

$\Rightarrow G_2 = \frac{1}{16} \times G_1 = \frac{1}{16} \times 4 = \frac{1}{4} \text{ } \Omega$

8.  $R = \frac{24}{6} = 4 \Omega$

$I = \frac{15}{4} + \frac{5}{4} = \frac{20}{4} = 5A$


$P_R = 5^2 \times 4 = 100W$

9.  $\frac{P_{\text{並}}}{P_{\text{串}}} = \frac{\frac{V^2}{R}}{\frac{V^2}{2R}} = 2 \times 2 = 4$

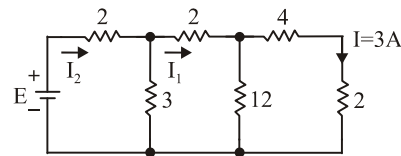10.  $I_1 = 3 + \frac{3 \times (4+2)}{12} = 3 + \frac{3}{2} = \frac{9}{2}A$

$I_2 = I_1 + \frac{2 \times \frac{9}{2} + 3 \times (4+2)}{3} = \frac{9}{2} + \frac{9+18}{3} = \frac{27}{2}A$

$E = 2 \times I_2 + 2 \times I_1 + (4+2) \times I = 27 + 9 + 18 = 54V$




11. 選擇 (15V, 2A)

$I = \frac{15}{6+3} + 2 \times \frac{6}{6+3} = \frac{15}{9} + \frac{12}{9} = \frac{27}{9} = 3A$

12. (A) N 個節點，可列出 (N-1) 個方程式

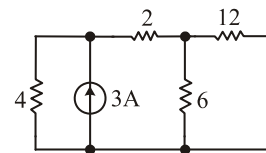13.  $V_{6\Omega} = 3 \times \frac{4}{4 + (2+6 \parallel 12)} \times \frac{12}{6+12} \times 6$   
 $= 3 \times \frac{4}{10} \times \frac{12}{18} \times 6 = 4.8V$



14.  $I_N = I_{ab} = (-I) \times \frac{6}{3+6} - (-I) \times \frac{3}{6+3} = -\frac{3}{9}I = -\frac{1}{3}I$


15.  $R_L = R_{th} = 4 \Omega$ ， $V_{RL} = V_{th} = -20 + 2 \times 4 = -12V$

$\therefore P_{RL} = \frac{V_{th}^2}{4 \times R_{th}} = \frac{(-12)^2}{4 \times 4} = \frac{12 \times 12}{4 \times 4} = 9(W)$

16.  $V_{ab} = 72 \times \frac{3}{18+6+3} + (-2) \times \frac{18}{18+(6+3)} \times 3$

$= \frac{72 \times 3}{27} - \frac{2 \times 18 \times 3}{27} = \frac{108}{27} = 4V$

17. (原電路)

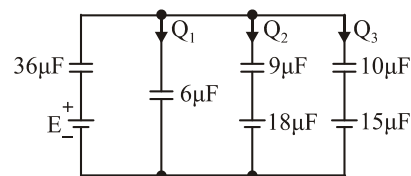

$Q_3 = 10 \mu \times 360 = 3600 \mu C$

$$Q_2 = (9//18) \times \frac{3600}{(10//15)} = 6 \times 600 = 3600 \mu\text{C}$$

$$Q_1 = 6 \times \frac{3600}{(10//15)} = 6 \times 600 = 3600 \mu\text{C}$$

$$E = \frac{Q_1 + Q_2 + Q_3}{(6+6+6)//36} = \frac{10800}{12} = 900 \text{ V}$$

$$18. W_C = \frac{1}{2} CV^2 = \frac{1}{2} QV = \frac{Q^2}{2C} = \frac{(4 \times 10^{-2})^2}{2 \times 20 \mu} = \frac{16 \times 10^{-4}}{40 \times 10^{-6}} = 40 \text{ J}$$

$$19. \vec{E}_A = \vec{E}_1 + \vec{E}_2 = E + (-E) = 0 \text{ V/m}$$

$$20. \frac{40 \text{ mH}}{L^2} = \left(\frac{600}{150}\right)^2 = 16 \Rightarrow L_2 = \frac{40 \text{ mH}}{16} = 2.5 \text{ mH}$$

$$21. L_{ab} = 8 + \frac{3 \times 6 - 3^2}{3+6+2 \times 3} = 8 + \frac{18-9}{9+6} = 8.6 \text{ H}$$

22. 佛來銘左手定則之左手之中指代表電流方向


$$23. V_C = 9 \times \frac{3}{6+3} = 3 \text{ V}$$

$$24. (A) \tau = \frac{L}{R}$$

$$(B) V_L(t) = E \cdot e^{-\frac{t}{\tau}}$$

$$(C) i(t) = \frac{E}{R} (1 - e^{-\frac{t}{\tau}})$$

25. 穩定  $\rightarrow$  L : 短路, C : 開路

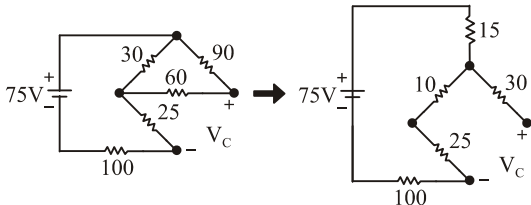

$$V_C = 75 \times \frac{(10+25)}{100+15+10+25} = 75 \times \frac{35}{150} = \frac{35}{2} = 17.5 \text{ V}$$

**第二部份：電子學**

26. 半導體作成的電阻其工作環境溫度上升時，其導電率增加

27. 空乏區內無電子與電洞存在，而障壁電位主要為施體與受體離子的作用

28. (D) 外接逆向偏壓時，所產生之漏電流，主因為少數載子的流動


$$29. R_f = \frac{0.8-0.6}{20 \text{ mA}} = 10 \Omega, V_D = 0.6 \text{ V}$$

$$V_o = (5-0.6) \times \frac{10}{10+40} + 0.6 = 1.48 \text{ V}$$

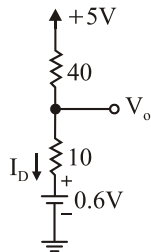30.  $D_1$  : ON,  $D_2$ 、 $D_3$  : OFF

$$\therefore I = \frac{(5-0.6-1)}{2} = 1.7 \text{ mA}$$

$$31. V_{2m} = \frac{110\sqrt{2}}{10} = 11\sqrt{2} \text{ V}$$



$$I_{(dc)} = \frac{V_{dc}}{5} = \frac{\frac{2}{\pi} \times 11\sqrt{2}}{5} = 1.98 \text{ mA}$$

32. 全波整流濾波：

$$r\% = \frac{2.4}{R_L \times C} \Rightarrow 0.05 = \frac{2.4}{10 \times C} \Rightarrow C = 4.8 \mu\text{F}$$

33. 當  $V_i + 2 \text{ V} < 0 \text{ V}$ ，即  $V_i < -2 \text{ V}$

則  $D$  : ON  $\Rightarrow V_o = V_i + 2 \text{ V}$

反之， $V_i > -2 \text{ V}$ ， $D$  : OFF， $V_o = 0 \text{ V}$

34. 分壓偏壓電路近似分析過程未用到  $\beta$  值，基極電壓  $V_B$  僅由  $V_{CC}$  與分壓電阻決定

35. 共集極電路電壓增益略小於 1

$$36. 10.7 = (2.5 + 0.5) \times (1 + 49) \times I_B + 50 \times I_B + 0.7$$

$$10 = 200 \times I_B \Rightarrow I_B = 0.05 \text{ mA}$$

$$\Rightarrow I_E = (1 + 49) \times I_B = 2.5 \text{ mA}$$

$$V_B = 0.7 \text{ V} + I_E \times R_E = 0.7 + 2.5 \times 0.5 = 1.95 \text{ V}$$

$$37. -0.7 = 5 \times I_E - 8 \Rightarrow I_E = \frac{8-0.7}{5} = \frac{7.3}{5} = 1.46 \text{ mA}$$

$$I_C \doteq I_E = 1.46 \text{ mA}$$

$$V_{CE} = (12 - (-8)) - (1+5) \times 1.46 = 11.24 \text{ V}$$

38. 欲使 LED ON  $\Rightarrow$  BJT  $\rightarrow$  飽和區

$$\therefore I_C \leq \beta I_B \Rightarrow \frac{12-1.8-0.2}{R_C} \leq 50 \times \frac{5-0.7}{R_B}$$

$$\Rightarrow \frac{R_B}{R_C} \leq 21.5 \left( \frac{R_B}{R_C} = \frac{5}{0.25} = 20 \right)$$

$$39. Z_i = R_B + r_\pi + (1 + \beta) \times R_E = R_B + (1 + \beta)(r_e + R_E)$$

$$40. A_v = \frac{V_o}{V_i} = -\beta \times \frac{R_C // R_L}{r_\pi} = -150 \times \frac{(5//10)}{1.25}$$

$$= -150 \times \frac{(\frac{10}{3})}{1.25} = -\frac{500}{1.25} = -400$$

$$41. Z_i = r_\pi + (1 + \beta) \times R_E = 1 + (1 + 99) \times 1 \doteq 100 \text{ k}\Omega$$

$$A_i = \frac{I_o}{I_i} = \frac{I_o}{i_b} \times \frac{i_b}{I_i} = (1 + \beta) \times \frac{R_B}{R_B + Z_i}$$

$$= (1 + 99) \times \frac{150}{150 + 100} = 60$$

$$42. V_B = 20 \times \frac{10}{90+10} = 2 \text{ V}, R_B = 90//10 = 9 \text{ k}\Omega$$

$$I_B = \frac{2-0.7}{9+(1+90) \times 1} = 0.013 \text{ mA}, r_\pi = \frac{26 \text{ mV}}{I_B} = 2 \text{ k}\Omega$$

$$A_v = \frac{V_o}{V_i} = -\beta \times \frac{R_C // R_L}{r_\pi} = -90 \times \frac{5//4}{2} = -100$$

$$43. 10 \text{ dBm} = 10 \times \log \frac{P_o}{1 \text{ m}} \Rightarrow P_o = 10 \text{ mW}$$

$$\Rightarrow P_o = \frac{V_o^2}{2.5} = 10 \Rightarrow V_o = 5 \text{ V}$$

$$A_{v1} = 20 = 20 \times \log \left( \frac{V_x}{V_i} \right) \Rightarrow \frac{V_x}{V_i} = 10$$

$$\Rightarrow V_i = \frac{V_x}{10} = \frac{50 \text{ mV}}{10} = 5 \text{ mV}$$

$$\therefore A_{VT} = 20 \times \log \left| \frac{V_o}{V_i} \right| = 20 \times \log \left( \frac{5}{5 \text{ m}} \right)$$

$$= 20 \times 3 = 60 \text{ dB}$$

44. RC 耦合串級放大器中，耦合電容主要功用為阻隔輸入訊號之直流成分

45. 共射極電晶體放大器之低頻響應部分主要受到射極旁路電容影響

46. (D) BJT 之操作速度較 FET 為快

47. (C)  $V_{GS} = 5 - 4.5 = 0.5 \text{ V} < V_{GS(OFF)} = 3.5 \text{ V}$   
 $V_{GD} = 5 - 3.5 = 1.5 \text{ V} < V_{GS(OFF)} = 3.5 \text{ V} \Rightarrow$  歐姆區

$$48. V_{GS} = 12 \times \frac{300}{300 + 600} - I_D \times 1 = (4 - I_D)$$

$$I_D = 4 \times \left( 1 - \frac{(4 - I_D)}{-2} \right)^2 = 4 \times \left( 3 - \frac{I_D}{2} \right)^2$$

$$= 4 \times \left( 9 - 3I_D + \frac{1}{4}I_D^2 \right) = 36 - 12I_D + I_D^2$$

$$\Rightarrow I_D^2 - 13I_D + 36 = 0 \Rightarrow I_D = \frac{13 \pm \sqrt{13^2 - 4 \times 36}}{2}$$

$$= 4 \text{ mA 或 } 9 \text{ mA (不合)}$$

$$\therefore V_{DS} = 12 - I_D \times (R_D + R_s) = 12 - 4 \times (1.5 + 1) = 2 \text{ V}$$

$$49. V_{GS} = V_{DS} = 10 - 3 \times (1 + R_s) = (7 - 3 \times R_s)$$

$$I_D = k \times (V_{GS} - V_t)^2 \Rightarrow 3 = 0.75 \times ((7 - 3R_s) - 2)^2$$

$$\Rightarrow 4 = (5 - 3R_s)^2 \Rightarrow R_s = 1 \text{ k}\Omega$$

50. N 通道增強型 FET 不適用自給偏壓法電路，因無法產生汲極電流  $I_D$